


Operational Amplifiers:-

Gives large output



May not be enough

∴ Cascade multiple amplifiers together

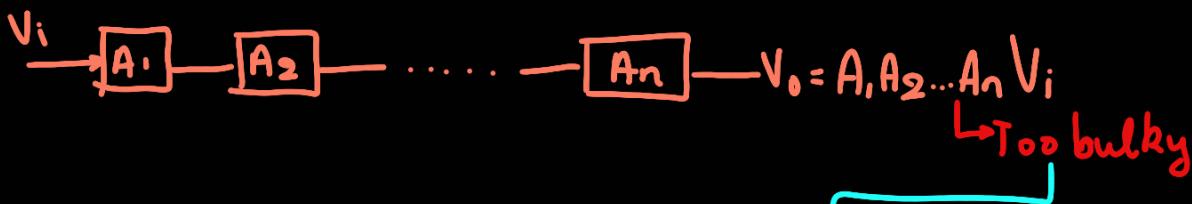

We need something just like this
but a Single integrated circuit

Op-Amp :-

↳ Has a very high gain integrated into a single circuit

Operations:-

Mathematical (Arithmetic)

Logical

Relational

coz its continuous

↳ Analog


Circuit

↳ Op-Amp is

a linear circuit

Cancels
the Common
DC voltage

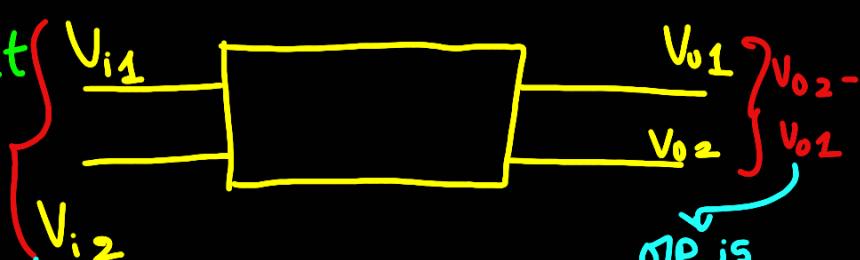
Has a very high gain &
capable of performing certain
operations like mathematical, logical
& relational.



∴ Differential I/P & Differential O/P

OP is
balanced

Different amplifiers :-

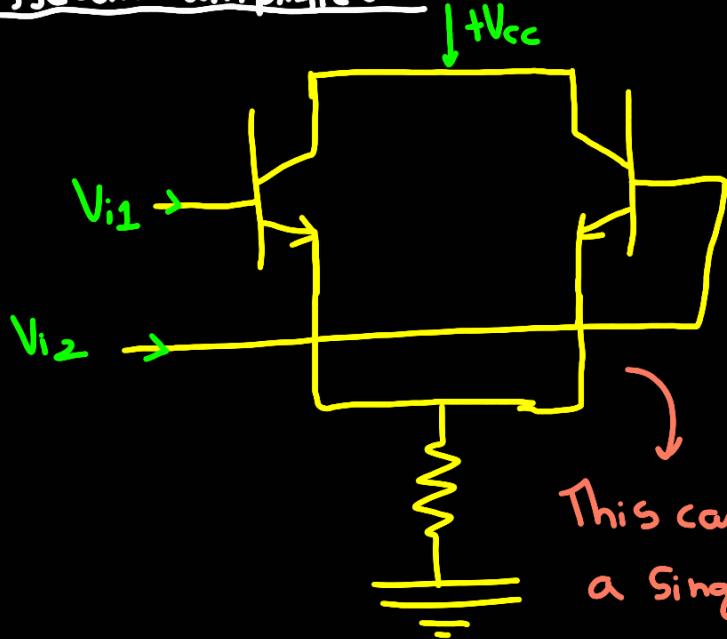


Capacitors &
Biasing resistors
eliminated

This can be integrated into
a Single chip.

Cascading


Symbol :-

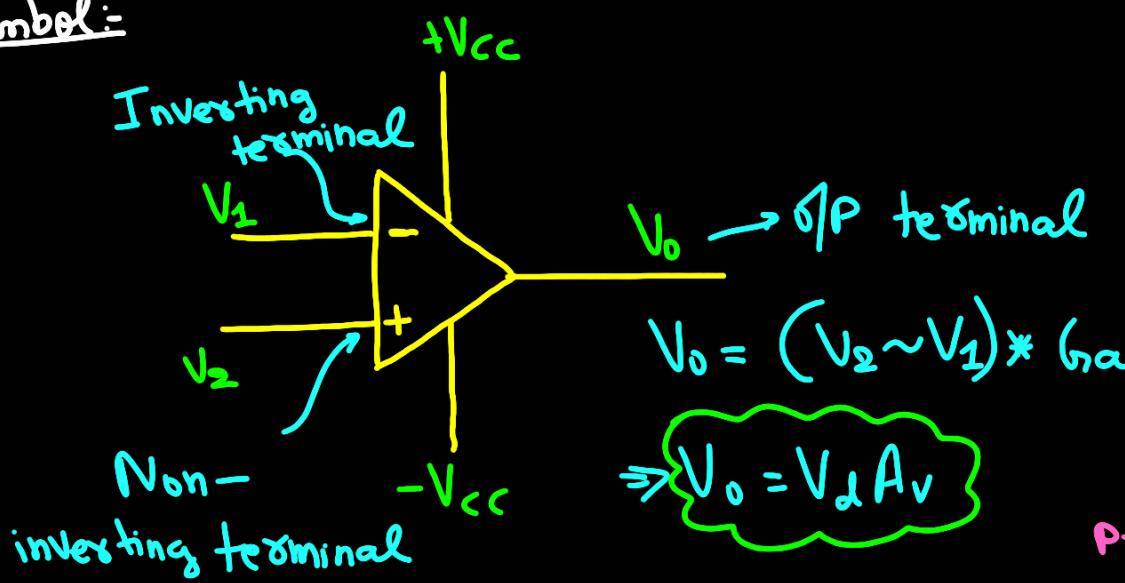

$$V_o = V_d A_v$$

Provides
current &
Voltage swing
by the load

Block diagram of op-Amp :-

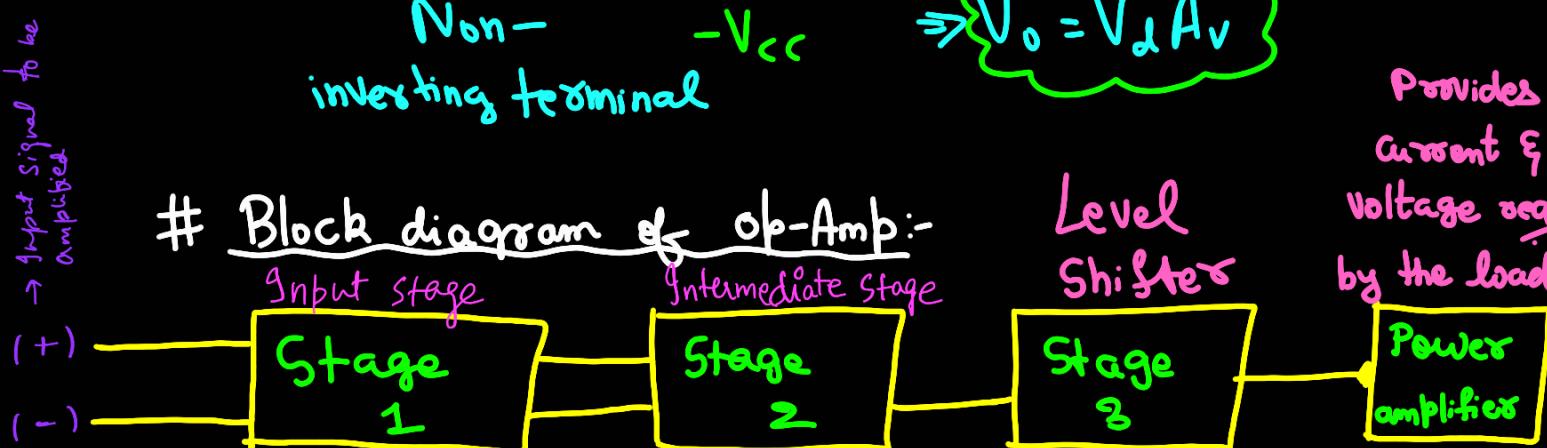

1. It's a differential amplifier
2. It's a dual input, balanced output
- Diff. Amp. (*DUAL O/P*)
3. Rejects noise
4. This stage also provides high I/P impedance
5. Provides high voltage gain

1. Dual I/P (balanced) and unbalanced O/P amplifier.
2. Provides very high voltage gain

1. The O/P of stage 2
- i.e I/P of stage 3 is above GND as direct coupling is used.
2. Level 3 (level shifter) is used to sift the O/P of level 2 downwards (wrt GND)

1. Also called as push pull amplifier
2. Increase the O/P voltage swing
3. Improves current supplying capabilities
4. Provides Min. O/P impedance

Voltage Transfer characteristics

Ideal Op-Amp VTC & its characteristics:-

★ ∞ i/p impedance ↴

Ideally no loading needed

★ Zero o/p impedance ↴

O/P can drive ∞ no. of other devices

★ ∞ Bandwidth ↴

So, that any freq. can be accepted by the ideal op-amp

★ ∞ Voltage gain

★ Perfect Balance, i.e. input offset voltage = 0

(If no i/p no o/p at all IDEALLY)

★ ∞ CMRR (Common Mode Rejection Ratio)

Differential Gain

Common Mode Gain

↳ If both the input signals are same or grounded, then diff. i/p is 0, ∴ the output is also 0 ideally, but $\neq 0$, practically

★ ∞ Slew rate → Rate of change of o/p voltage w.r.t time = $\frac{dV_o}{dt}$


(Tells us how fast the amplification process takes place)

↳ Saturat' region
↳ It becomes an oscillator (constant gain)

↳ Saturat' region

↳ It becomes an oscillator (constant gain)

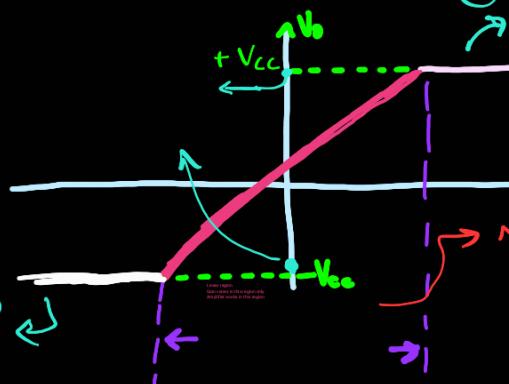Note: For an amplifier gain must keep on changing



↳ Saturat' region
↳ It becomes an oscillator (constant gain)



↳ Gain can be

reduced using
-Ve feedback

↳ Saturat' region
↳ It becomes an oscillator (constant gain)

↳ Note: For an amplifier gain must keep on changing

↳ Saturat' region
↳ It becomes an oscillator (constant gain)

↳ Note: For an amplifier gain must keep on changing

↳ Saturat' region
↳ It becomes an oscillator (constant gain)

↳ Note: For an amplifier gain must keep on changing

↳ Saturat' region
↳ It becomes an oscillator (constant gain)


↳ Note: For an amplifier gain must keep on changing

★ Op-Amp is
amplifier with
-Ve feedback

↳ Reduced using
-Ve feedback
↳ $I_S = -I_I$
 $O/P = -V_o$
O/P is always 180° out of phase

Applications of Op-Amp:-

① Inverting Amplifiers:-

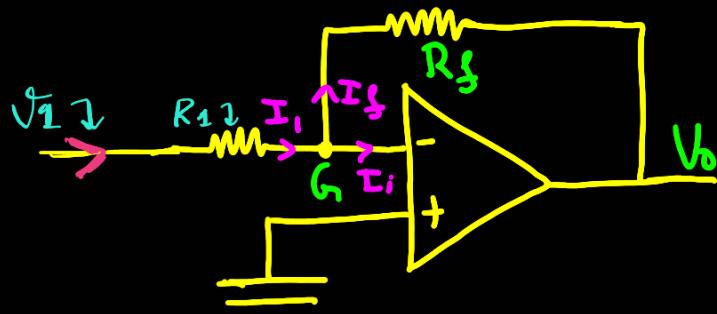

$$V_0 = A_v V_1$$

$$I_i = \frac{V_1 - V_G}{R_1}$$

$$V_G = 0$$

$$I_i = \frac{V_1}{R_1}$$

$$I_i = I_o + I_f \Rightarrow I_i = I_f$$

$$I_f = \frac{V_G - V_o}{R_f} = -\frac{V_o}{R_f}$$

$$-\frac{V_o}{R_f} = \frac{V_1}{R_1} \Rightarrow V_o = -\frac{R_f}{R_1} V_1 \rightarrow \text{O/P voltage}$$


$A_v = -\frac{R_f}{R_1}$ → Gain

* R_f : feedback resistance

* I_i : Inverting current

* I_1 : Net current

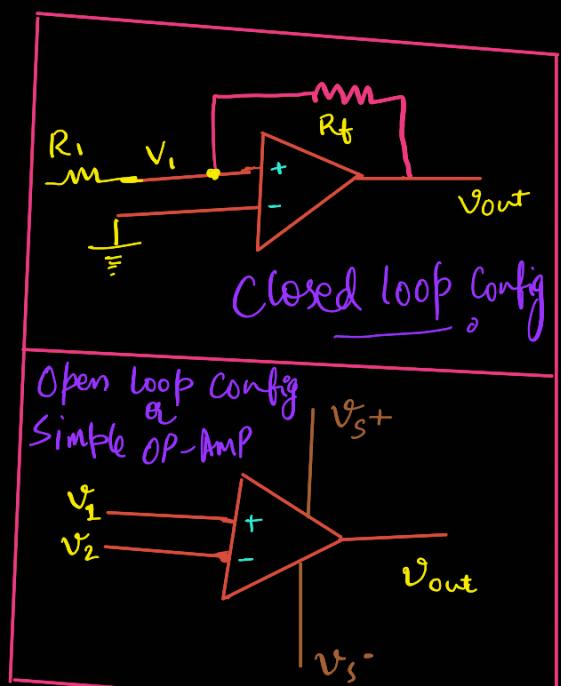- 1. Does not exist in electrical ckt, it exists only in Electronic ckt (op-amps)
- 2. Node whose voltage is zero but not connected to GND physically or mechanically.




The open loop gain is extremely high, and because of such high gain the OP AMP becomes unstable, so in order to avoid such conditions we connect a resistor (Rf) from output back to the input (closed loop OP AMP) to lose some gain, this helps us in reducing and controlling the gain. It depends on the value of the resistor (Rf).

Therefore, closed loop OP AMP is more controlled than open loop OP AMP.

O/P is inverted by a phase shift of 180°

Non-inverted amplifiers:-

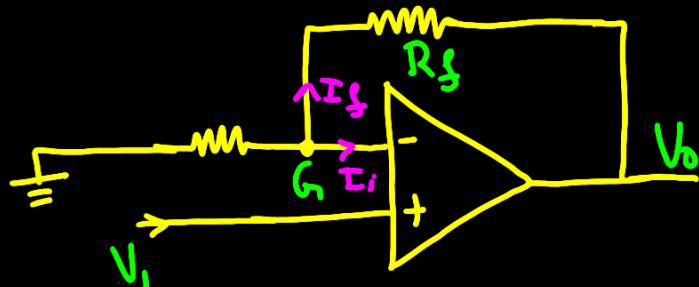


Follow same procedure for $V_0 \& A_v$

$$V_0 = \frac{R_f}{R_i} + 1 \rightarrow \text{O/P voltage}$$

$$A_v = \frac{R_f}{R_i} + 1 \rightarrow \text{Gain}$$

**O/P phase shift is $0/360^\circ$

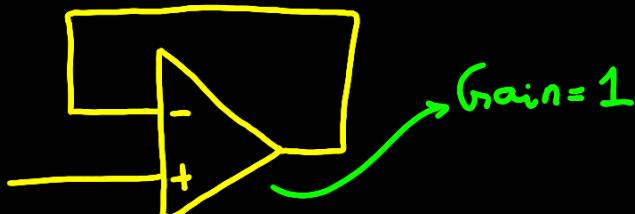Voltage Followers / Unity Gain Amplifiers / Buffer Amplifiers:-



$$\text{Non-inverting amplifier gain} = \frac{R_f}{R_i} + 1$$

Eliminating $R_f \Rightarrow A_v = 1$


$$\therefore V_0 = V_i \rightarrow \text{Thus, } V_0 \text{ follows } V_i$$

1. In buffer amplifier the O/P voltage follows I/P voltage, i.e. $V_{out} = V_{in}$
2. Loop gain = 1
3. It's a special case of *Non-inverting (+ve)* amplifier so phase of O/P signal is $0/360^\circ$
4. Feedback resistance (R_f) = 0
 $R_1 = \infty$


Application:

1. Adds buffer effect to the ckt
2. Used for impedance matching
3. Acts as an Isolator

Summing Amplifiers :-

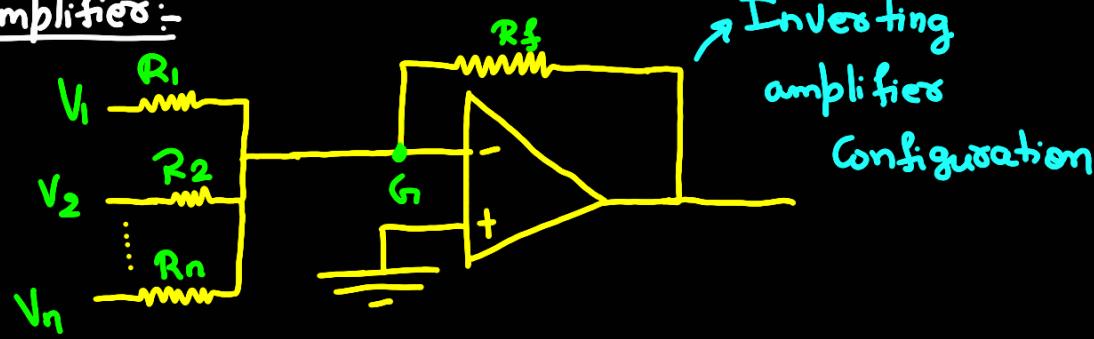

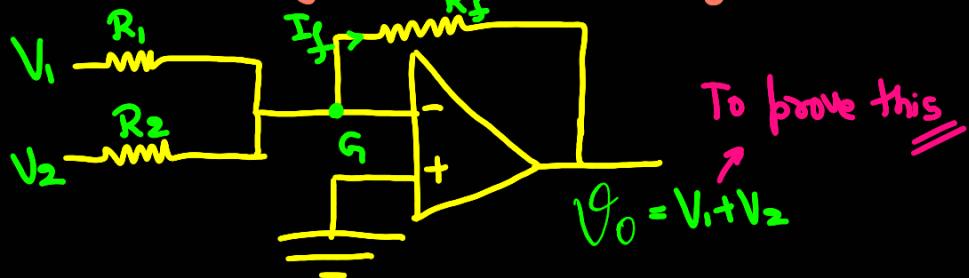For analysis, we consider only $V_1 \& V_2$



$$I_1 = \frac{V_1 - V_G}{R_1} = \frac{V_1}{R_1}$$

$$I_2 = \frac{V_2 - V_G}{R_2} = \frac{V_2}{R_2} \quad (V_G = 0)$$

* The sum of currents $I_1 \& I_2$ enters node G.


* Since I_i (current into op-amp) is zero $\Rightarrow I_f = I_1 + I_2$

$$I_f = \frac{V_G - V_0}{R_f} = \frac{-V_0}{R_f}$$


$$\frac{-V_0}{R_f} = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$

$$\text{Let } R_f = R_1 = R_2 = R$$

$$\Rightarrow -V_0 = V_1 + V_2 \Rightarrow | -V_0 | = V_1 + V_2 \quad \begin{array}{l} \text{Thus, it can be} \\ \text{used as adder circuit} \end{array}$$

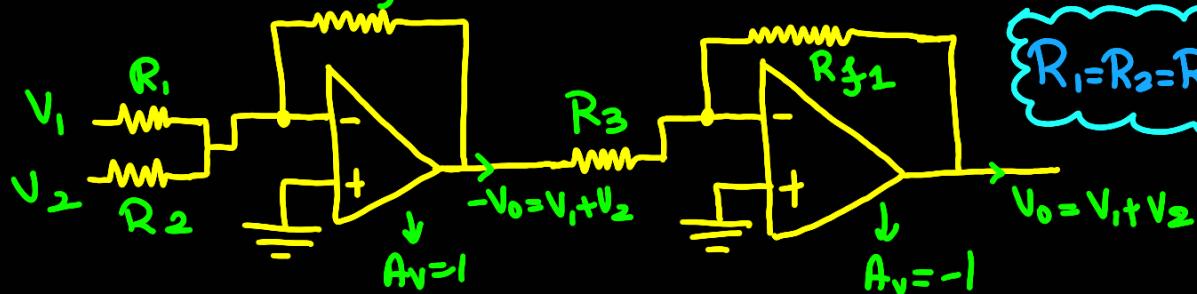

Subtractor :-

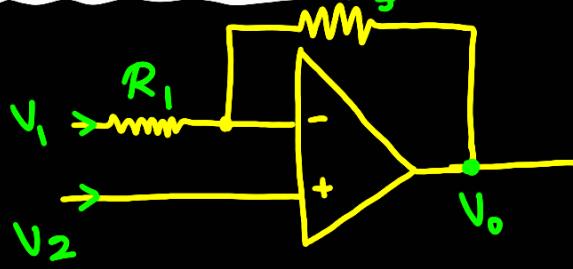

To prove :- $V_o = V_2 - V_1$

$$V_{o1} = -\frac{R_f}{R_1} (V_1)$$


$$V_{o2} = \left(1 + \frac{R_f}{R_1}\right) (V_2)$$

Taking $R_f = R_1 = 1$ $\Rightarrow V_{o1} = -V_1$ \rightarrow We need this

$\Rightarrow V_{o2} = 2V_2$ \rightarrow We don't need this

$\frac{1}{2}$ \rightarrow Thus we need to divide!

Use a \downarrow voltage divider

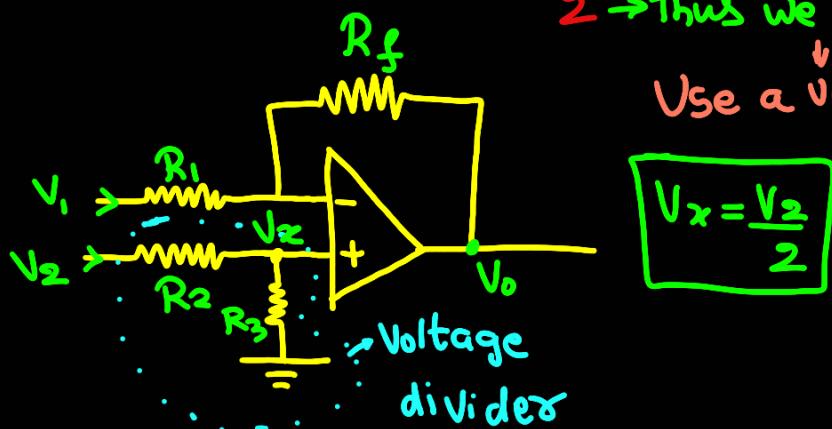

Expression for O/P voltage :-

O/P voltage due to V_1 is V_{o1} given by

$$V_{o1} = -\frac{R_f}{R_1} V_1 \rightarrow ①$$

O/P voltage due to V_2 is V_{o2} given by

$$V_{o2} = \left(1 + \frac{R_f}{R_1}\right) V_x \rightarrow ②$$

$$V_x = R_3 \left(\frac{R_2}{R_2 + R_3} \right) \rightarrow ③$$

Thus from ③, ② now becomes

$$V_x = \left(1 + \frac{R_f}{R_1}\right) \left(\frac{R_3 V_2}{R_2 + R_3} \right)$$

$$V_o = V_{o1} + V_{o2}$$

$$V_o = \frac{-R_f}{R_1} V_1 + \left(1 + \frac{R_f}{R_1}\right) \left(\frac{R_3}{R_2 + R_3}\right) V_2$$


Let $R_1 = R_2 = R_3 = R_f = R$

$$V_o = -\frac{R}{R} V_1 + \left(1 + \frac{R}{R}\right) \left(\frac{R}{R+R}\right) V_2 = -V_1 + V_2$$

$\therefore V_o = V_2 - V_1$ Thus it is used as a subtractor

Integrator:-

↳ Op-amp is used for integration

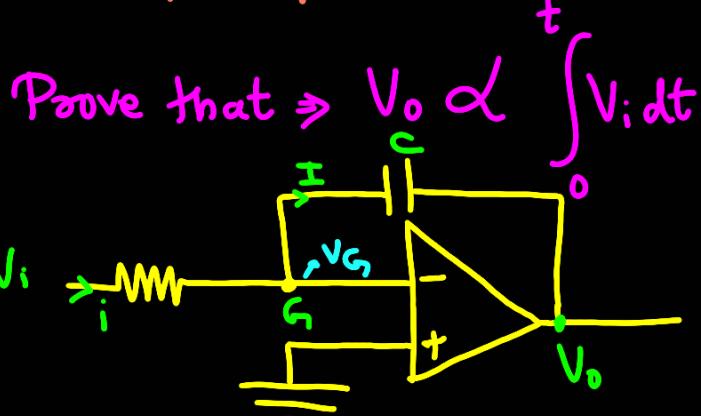

Voltage across capacitor C is $V_G - V_o = \frac{q_V}{C} \Rightarrow -V_o = \frac{q_V}{C}$ ①

$$\text{WKT} \Rightarrow q_V = \int_0^t i dt \rightarrow ②$$

From the ckt $i = \frac{V_i - V_G}{R} = \frac{V_i}{R}$ ③ ($V_G = 0$)

Put ③ & ② in ①

$$-V_o = \frac{1}{C} \int_0^t i dt = \frac{1}{C} \int_0^t \frac{V_i}{R} dt$$


$$V_o = -\frac{1}{RC} \int_0^t V_i dt$$

$\Rightarrow V_o \propto \int_0^t V_i dt$

Thus, it can be used as integrator

Differentiator :-

Op-Amp
used for
differentiation

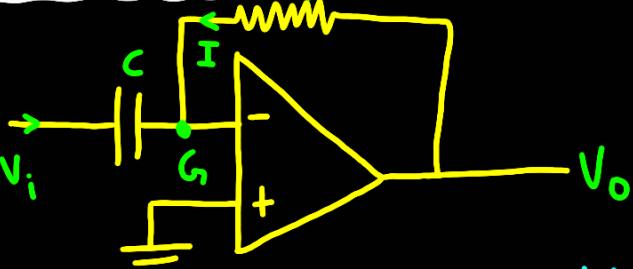

$$I = \frac{V_o - V_G}{R} = \frac{V_o}{R} \rightarrow \textcircled{1}$$

$$V_i - V_G = \frac{q}{C} \Rightarrow q = CV_i \rightarrow \textcircled{2}$$

$$\frac{1}{V_G} = 0$$

Differentiating $\textcircled{2}$, we get

$$\frac{dq}{dt} = C \frac{dV_i}{dt} \Rightarrow -\frac{V_o}{R} = C \frac{dV_i}{dt}$$

$$-V_o = RC \frac{dV_i}{dt}$$


$$V_o = -RC \frac{dV_i}{dt} \Rightarrow V_o \propto \frac{dV_i}{dt}$$

Thus it can be used as differentiator

Comparator :-

* Compare V_2 with V_1

V_1

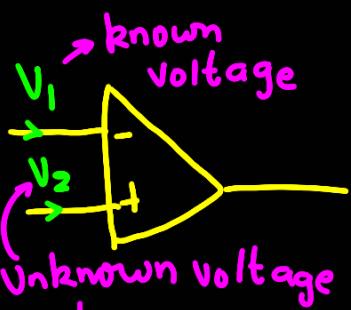


V_2


- * $V_2 < V_1 \Rightarrow$ O/P is -Ve
- * $V_2 > V_1 \Rightarrow$ O/P is +Ve

| * $V_2 = V_1 \Rightarrow$ O/P is Zero


Voltage to Current converters:-

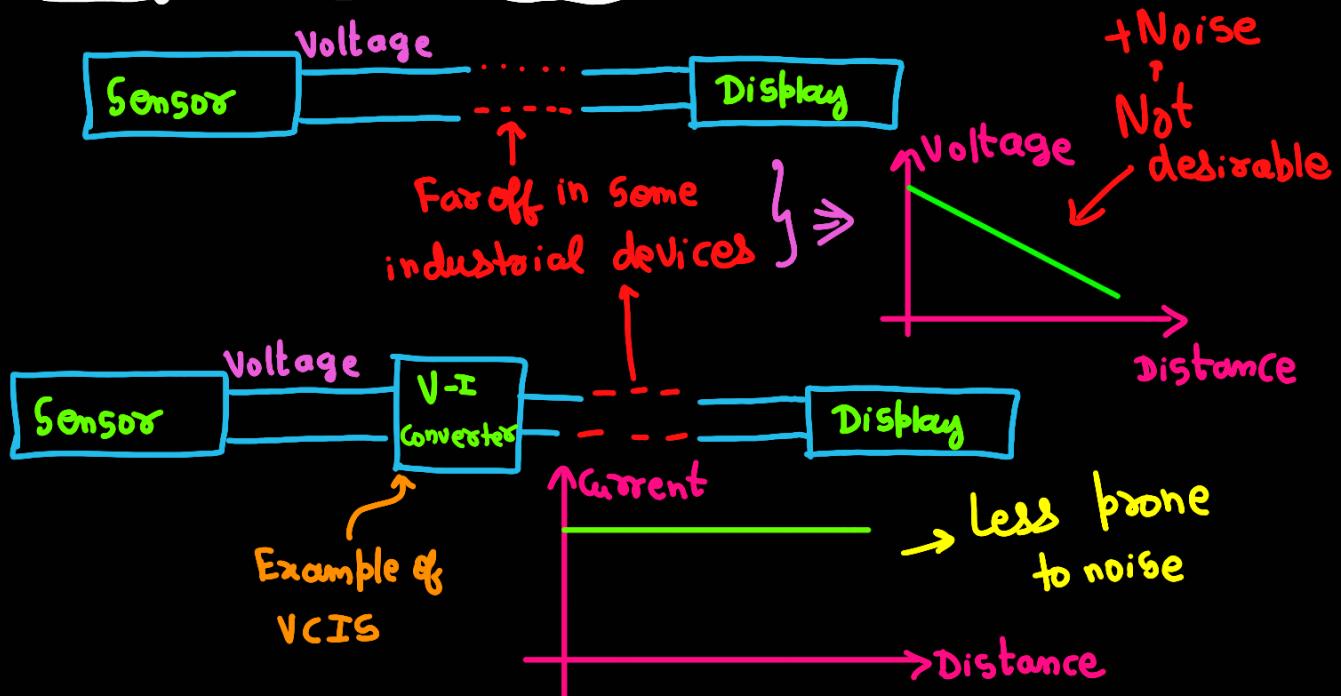

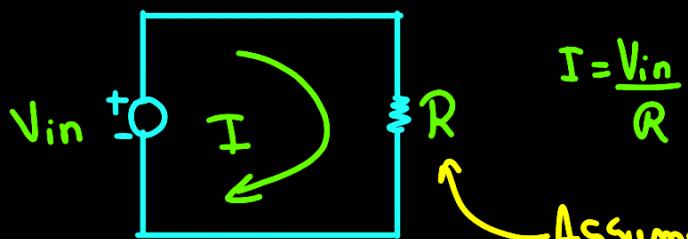→ V-I converters using passive components (Passive converter) :-




Assumed to have no voltage drop

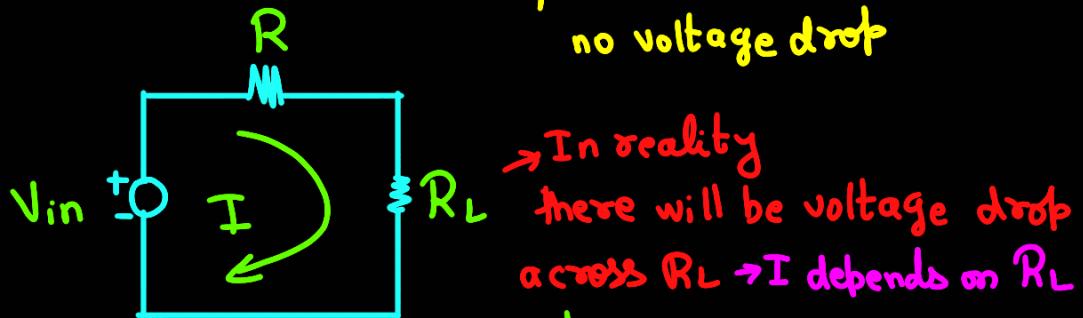

In reality there will be voltage drop across $R_L \rightarrow I$ depends on R_L
↓
Opamps fix this issue

→ Active V-I converter :-

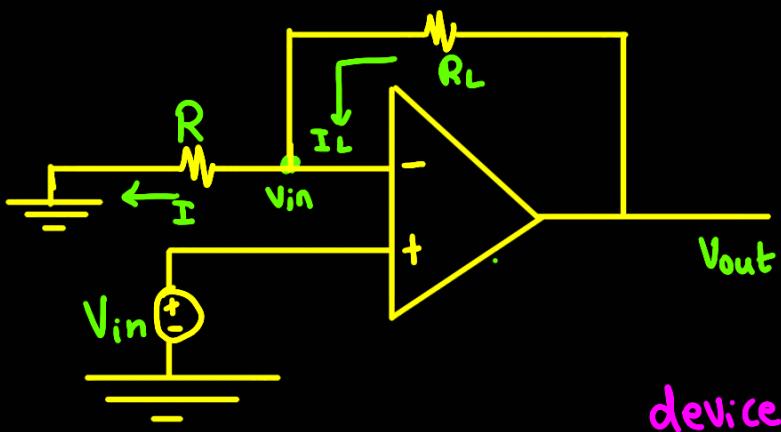↳ AKA floating load converter ^{Load is floating}



Applying KCL

$$I = I_L$$


$$\frac{V_{in}}{R} = I_L$$

$$\Rightarrow I_L \propto \frac{V_{in}}{R}$$

Setting R , the device behaved as V-I converter

- This type of ckt is used to drive LEDs
- Also used to find matched pairs of diodes or Zener diodes

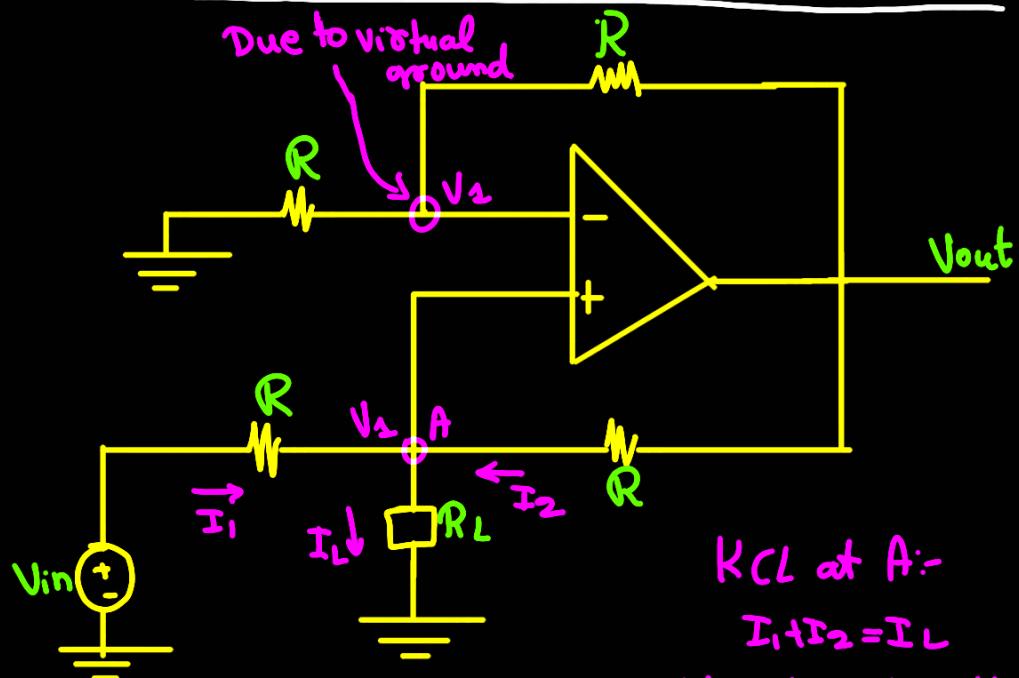⇒ Ground Load Voltage to Current converter



KCL at A:-

$$I_1 + I_2 = I_L$$

$$\frac{V_o - V_1}{R} + \frac{V_{out} - V_1}{R} = I_L$$

$$V_{in} + V_o - 2V_1 = I_L \times R$$

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

$$V_o = \left(1 + \frac{R}{R_1}\right) V_{in} \Rightarrow \boxed{V_o = 2V_{in}}$$

$$\Rightarrow V_{in} + 2V_{in} - 2V_1 = I_L \times R$$

$$\boxed{I_L = \frac{V_{in}}{R}}$$


$I_L \propto V_{in}$

once R is set



↳ independent of R_L

↳ This way it works as V-I converter

Current to Voltage converter :-

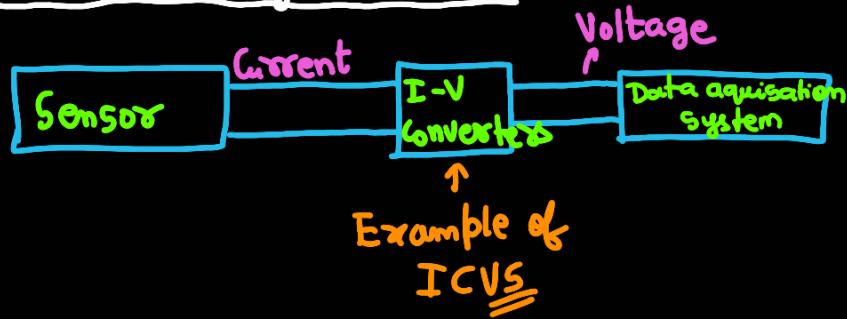


* Passive I-V converter :-

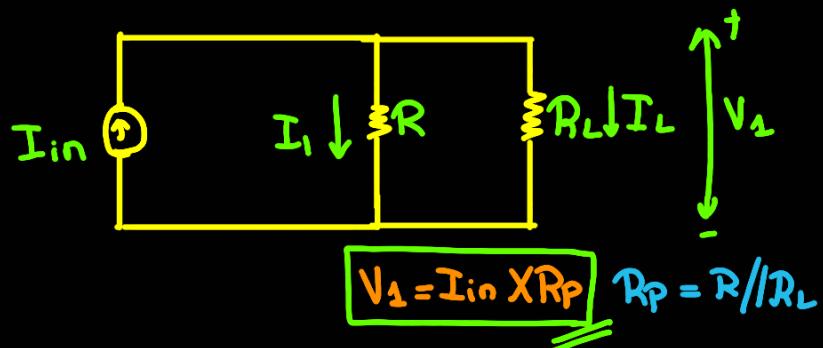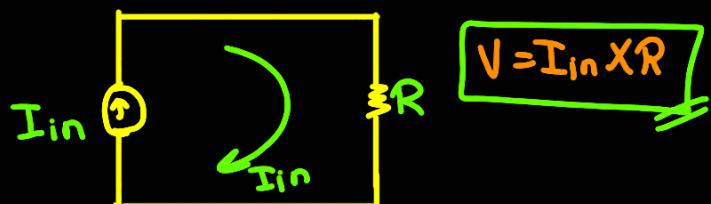


Actual voltage appearing across R_L is less than the converted voltage
This is fixed by op-amps

* Active I-V converter :-

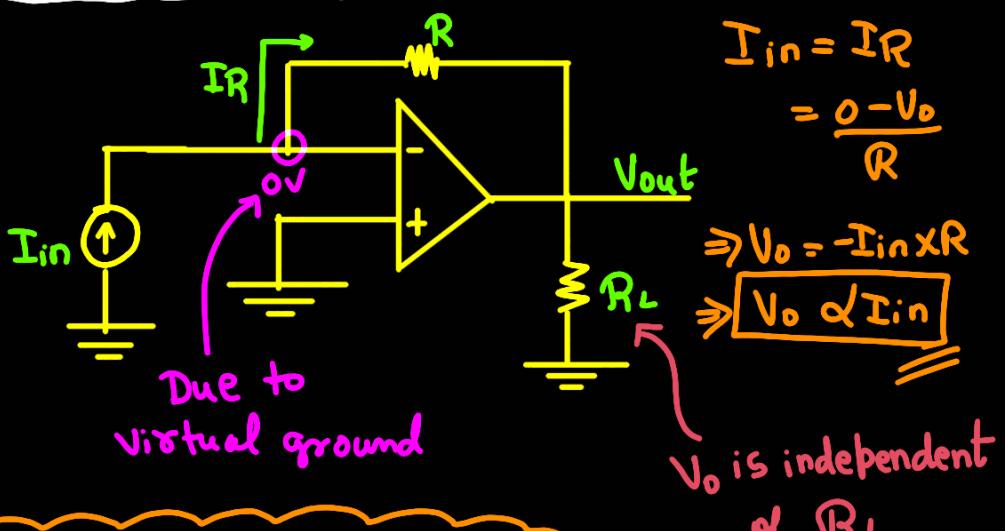


AKA Transimpedance Amplifier

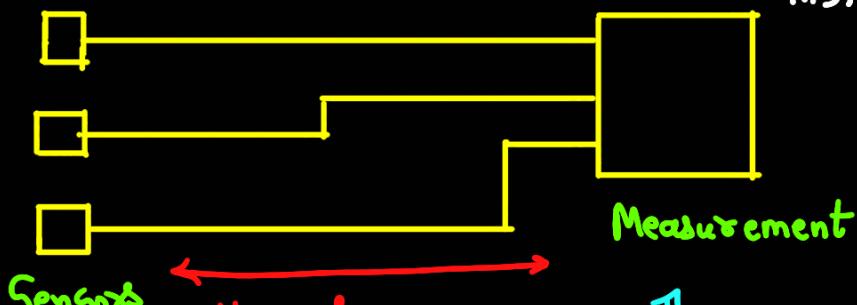Op-Amp as differential amplifiers :- Why should it be replaced by instrumentation amplifiers?



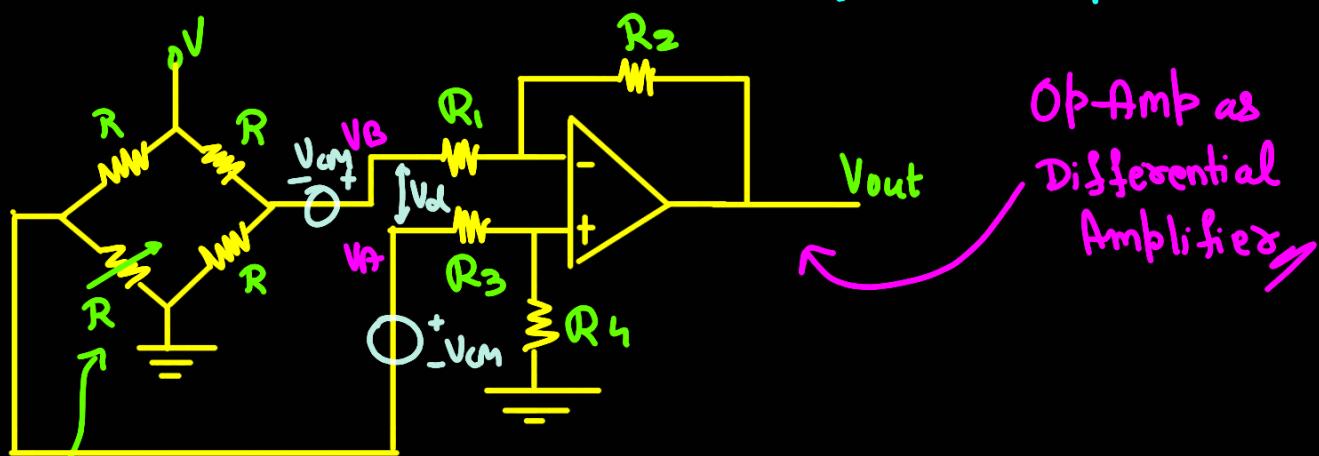Thus we use
→ Poone to noise differential amplifiers



Std Bridge ckt
of sensors

V_A & V_B are voltages that appear at the two terminals
of the differential amplifier

$$\therefore V_o = \frac{R_4}{R_3 + R_4} \times \left(1 + \frac{R_2}{R_1} \right) V_A - \frac{R_2}{R_1} V_B$$

$$V_o = \frac{R_4 \times V_A}{R_3} \left[\frac{1 + \frac{R_2}{R_1}}{1 + \frac{R_4}{R_3}} \right] - \frac{R_2}{R_1} \times V_B$$

If we assume $\frac{R_4}{R_3} = \frac{R_2}{R_1} \Rightarrow V_o = \underbrace{\frac{R_2}{R_1} (V_A - V_B)}$
O/P is difference of i/p multiplied by the gain of the ckt.


If V_{cm} is present

↳ Common mode voltage

$$\Rightarrow V_o = A_d V_d + A_c V_{cm}$$


Mismatch in Resistors (say 1% error) causes change in V_o
↓
Undesirable

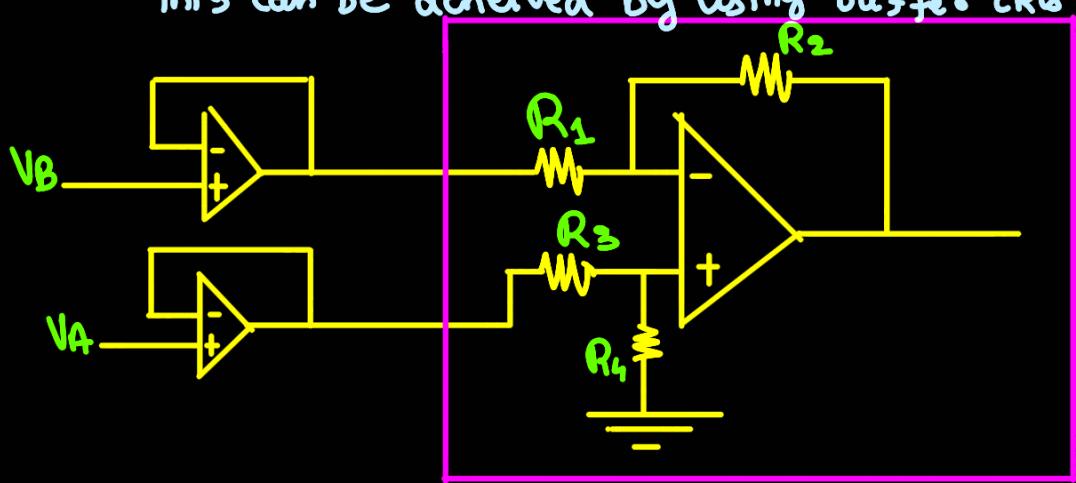The i/b impedance of the diff amplifiers must be very high.
This can be achieved by using buffer ckt's in i/b



The gain of these
ICs cannot be changed
This is fixed by
replacing buffer ckt's
with the non-inverting amplifiers

Inside structure
of monolithic ICs

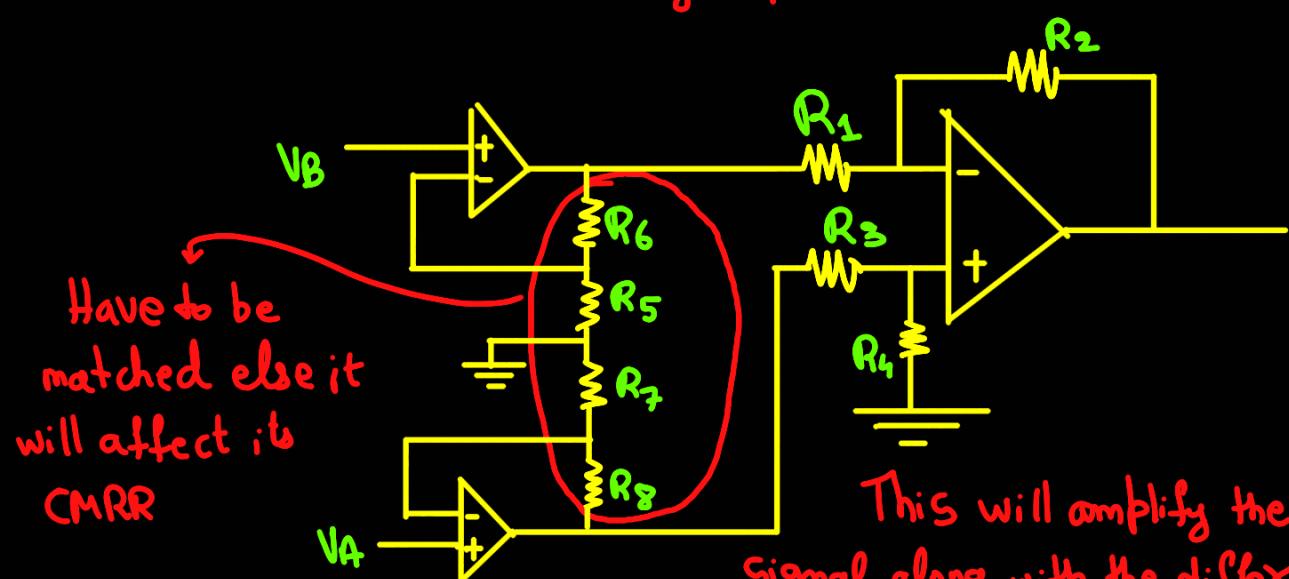


Have to be
matched else it
will affect its
CMRR

This will amplify the common mode
Signal along with the differential signal.

No improvement in the signal to noise ratio

All of these are solved by
instrumentation amplifiers ☺

Instrumentation Amplifiers :-

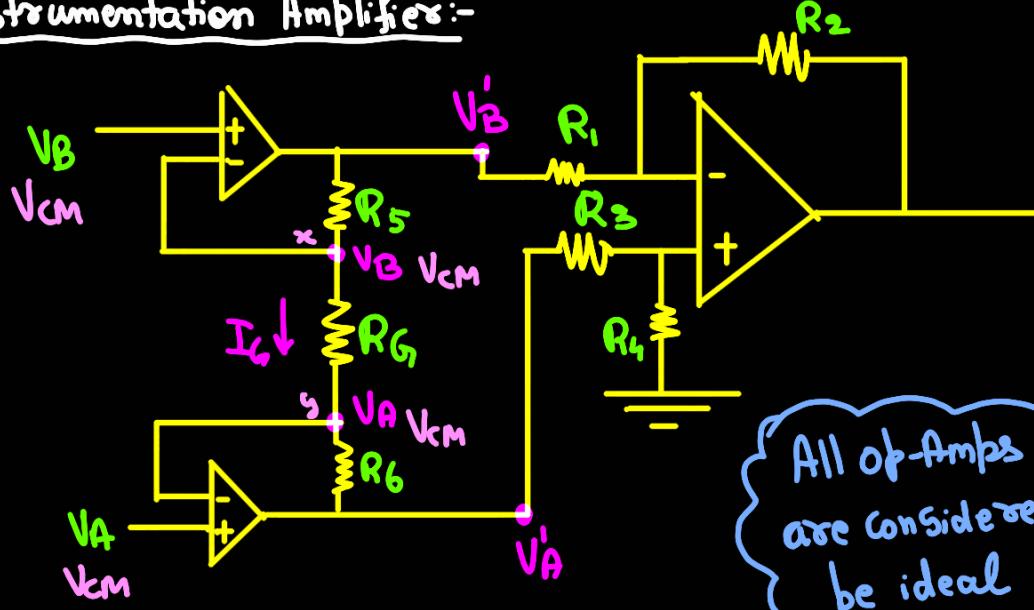

R_G is common to both the Op-Amps.

Advantage \rightarrow Amplifies only differential input signal.

Available as an IC \Rightarrow All resistors except R_G is fabricated internally

↳ Gain can be set by setting R_G externally

★ Deriving expression for V_D :-

$$V_{out} = \frac{R_2}{R_1} (V_A' - V_B') \text{ if } \frac{R_4}{R_3} = \frac{R_2}{R_1}$$

$$I_G = \frac{V_B - V_A}{R_G} \rightarrow \text{This flows through } R_5, R_6 \text{ & } R_G$$

$$V_B' - V_A' = I_G (R_5 + R_6 + R_G)$$

If $R_5 = R_6$

$$\Rightarrow V_B' - V_A' = I_G (2R_5 + R_G)$$

$$V_B' - V_A' = (V_B - V_A) \left[1 + \frac{2R_5}{R_G} \right] \Rightarrow V_A' - V_B' = V_A - V_B \left(1 + \frac{2R_5}{R_G} \right)$$

$$V_o = \left(\frac{R_2}{R_1} \right) (V_A' - V_B')$$

$$\Rightarrow V_o = \frac{R_2}{R_1} \left(1 + \frac{2R_5}{R_6} \right) (V_A - V_B)$$

Understanding how the first two amplifiers pass CM voltage :-

V_{CM} → Common Mode Voltage.

V_{CM} is present at nodes $x, x', y \& y'$ as well

∴ No current will flow through R_6

∴ No current will flow through $R_5 \& R_6$

For common mode voltage, these 2 op-Amps act as buffers

∴ V_{CM} will not be amplified

Only i/p diff. i/p will be amplified

→ CMRR can be further increased by this amplifier

→ Particularly useful when i/p diff. signal is small & $V_{diff} < V_{cm}$


Log & Anti log amplifiers :-

By Using logarithmic properties of ckt elements the following can be achieved


$$\star \log(AB) = \log(A) + \log(B) \quad \star \log(A^B) = B \log(A)$$

$$\star \log\left(\frac{A}{B}\right) = \log(A) - \log(B)$$

For example:-

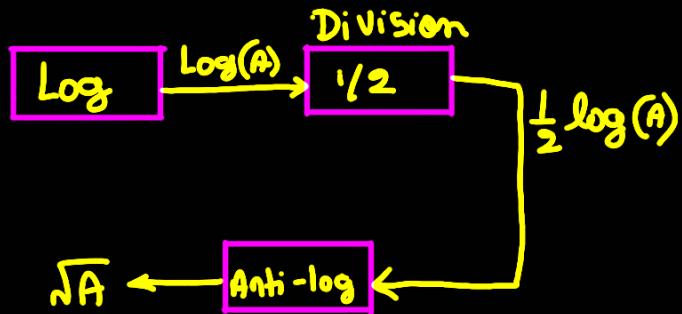

* Log Amplifier using Op-Amp & Diode :-

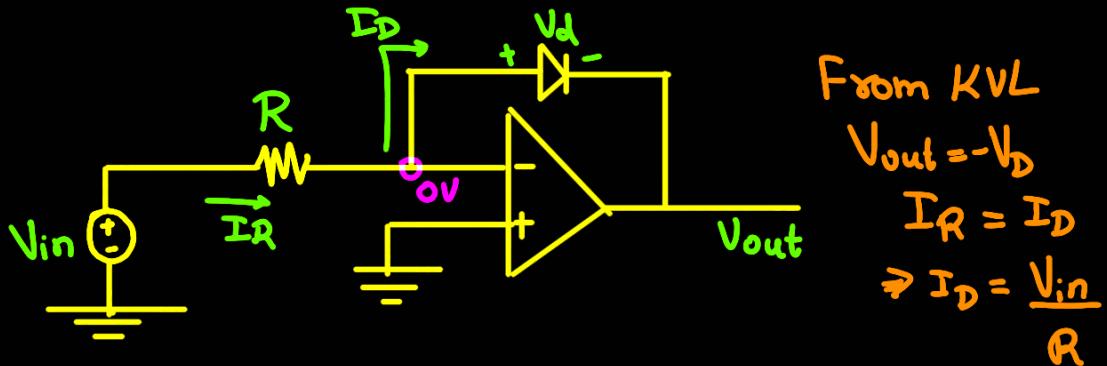

From KVL

$$V_{out} = -V_D$$

$$I_R = I_D$$

$$\Rightarrow I_D = \frac{V_{in}}{R}$$

We know from current eqn of diode

$$I_D = I_S \left(e^{\frac{V_D}{\eta V_T}} - 1 \right) \rightarrow V_T = \frac{kT}{q} \quad V_T = 26 \text{ mV at room temp.}$$

I_S - Reverse Saturation Current

V_T - Thermal Voltage

V_D - Forward Voltage of Diode

η - Ideality Factor $\begin{cases} 1 \text{ for Si} \\ 2 \text{ for Ge} \end{cases}$

$$\text{For the log amp above} \Rightarrow I_D = I_S \left(e^{\frac{V_D}{\eta V_T}} - 1 \right)$$


$$I_D = I_S \left(e^{\frac{V_D}{\eta V_T}} \right) \Rightarrow \frac{I_D}{I_S} = e^{\left(\frac{V_D}{\eta V_T} \right)}$$

Taking natural log on both sides

$$\ln \left(\frac{I_D}{I_S} \right) = \frac{V_D}{\eta V_T} \Rightarrow V_D = \eta V_T \ln \left(\frac{I_D}{I_S} \right)$$


$$V_D = -V_D \Rightarrow V_{out} = -\eta V_T \times \ln \left(\frac{V_{in}}{I_S \times R} \right) \rightarrow \text{O/P voltage.}$$

Analog amplifiers using diode :-

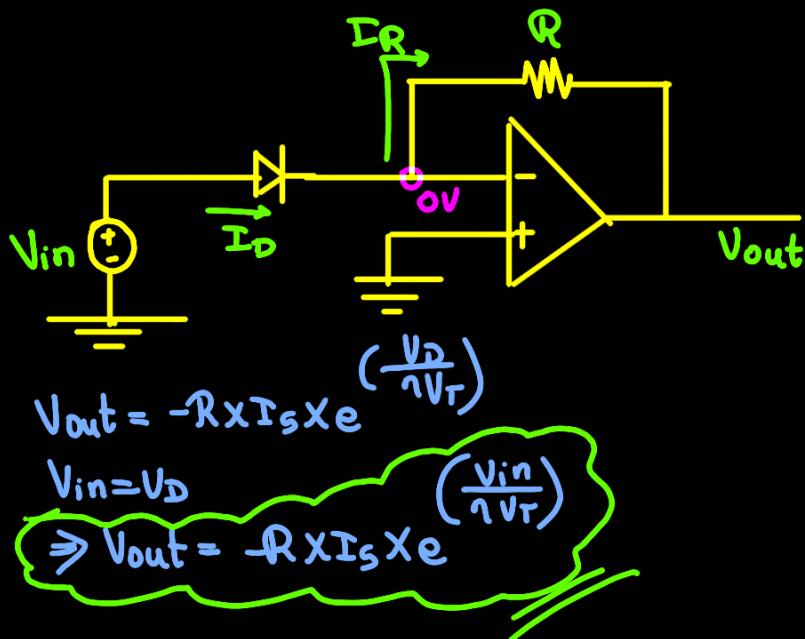


$\eta \Rightarrow$ The dynamic range of the amplifier reduces due to η
 ↳ Fixed by transistor base log & anti-log amplifiers

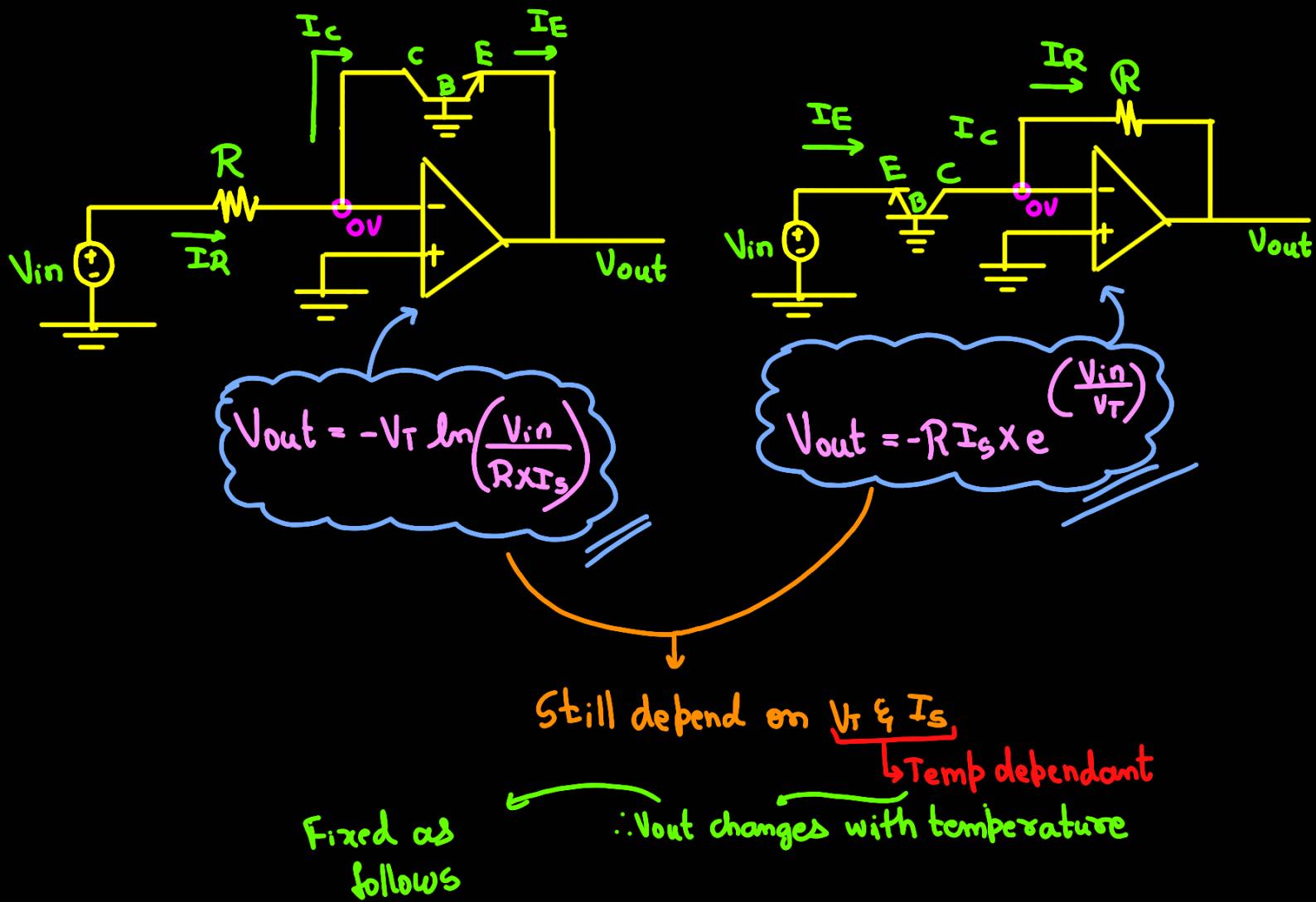Log & Anti-log amplifiers using Op-Amp & Transistor :-



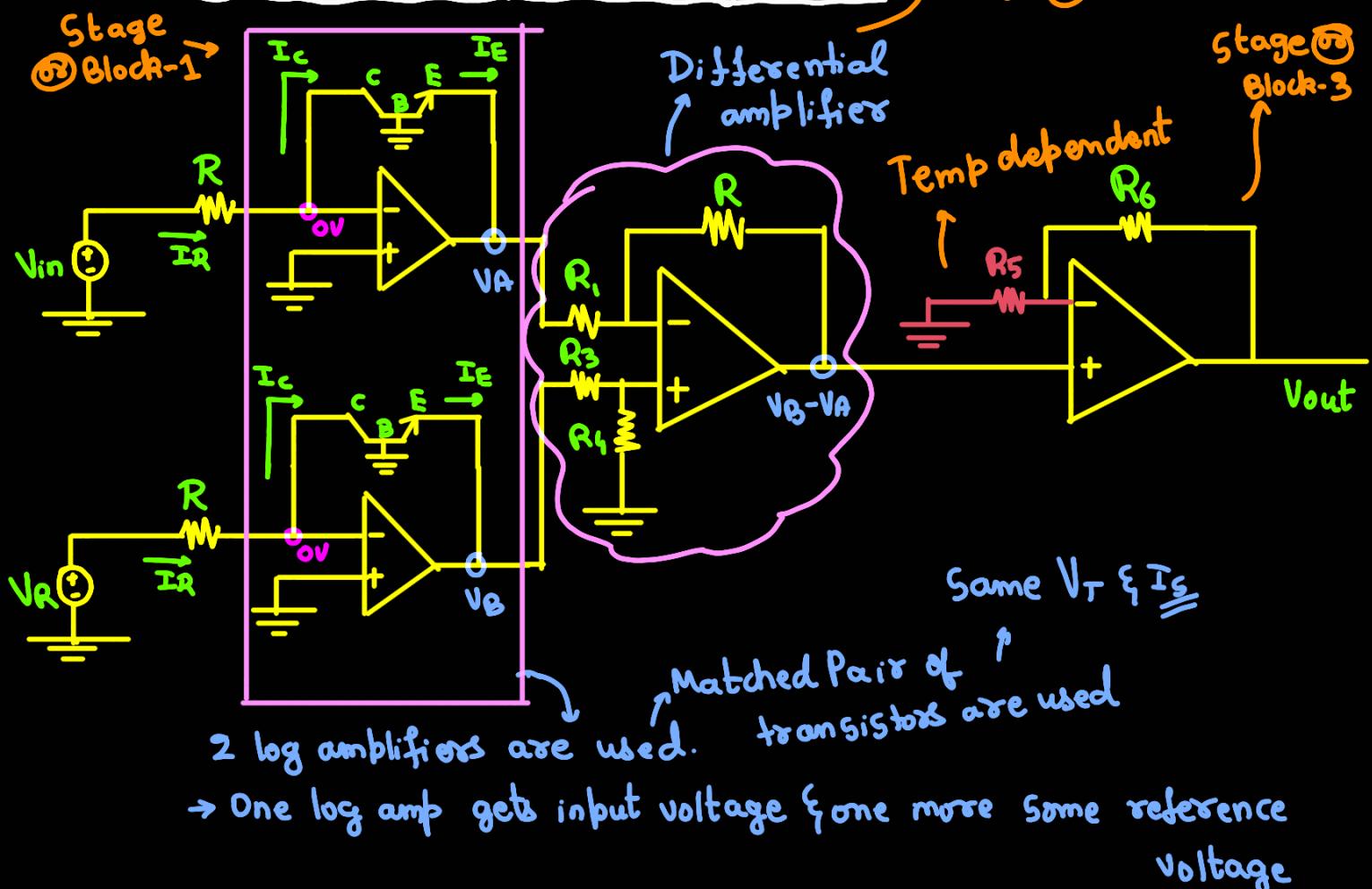Temperature Compensated Log Amplifier :- Stage @ Block-2



$$V_A = -V_T \times \ln\left(\frac{V_{in}}{R \times I_S}\right) \quad | \quad V_B = V_T \times \ln\left(\frac{V_R}{R \times I_S}\right)$$

$$V_B - V_A = V_T \times \ln\left(\frac{V_{in}}{R \times I_S}\right) - V_T \times \ln\left(\frac{V_R}{R \times I_S}\right)$$

$$\Rightarrow V_B - V_A = V_T \ln\left(\frac{V_{in}}{V_R}\right) \rightarrow \text{Independent of } I_S$$

But still depends

\hookrightarrow 3rd Block fixes

Non-inverting op-Amp,,


This is how temp. T is compensated

$$V_0 = \left(1 + \frac{R_b}{R_s}\right) \times V_T \times \ln\left(\frac{V_{in}}{V_R}\right) \rightarrow \text{By choosing temp. coeff. of } R_s \\ \text{we can nullify effect of } V_T$$

Precision Rectifier :-

- Half-wave rectifiers ckt rectifies in real condⁿ only after a certain threshold voltage V_T
- This is not affected in large signal operation, but in small Signal conditioning & signal processing/AM demodulation, it affects a lot

Precision Rectifiers solve this problem

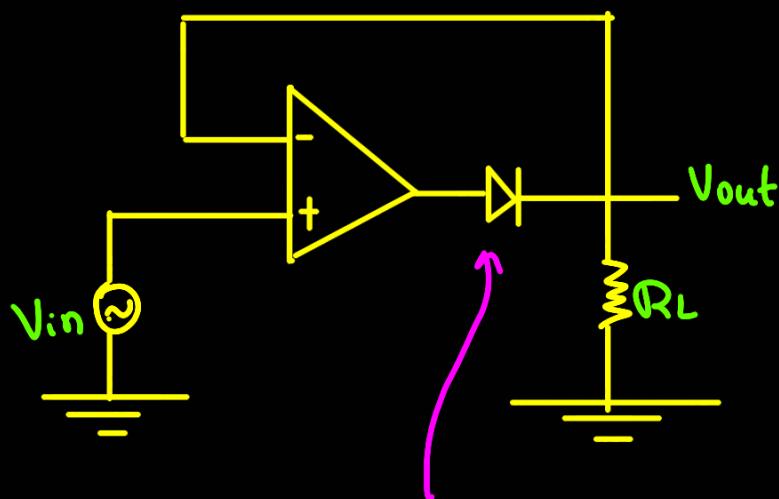


Here diode behaves as ideal
⇒ Rectifier = ideal

Transfer characters:-

Precision rectifier


Half wave rectifier

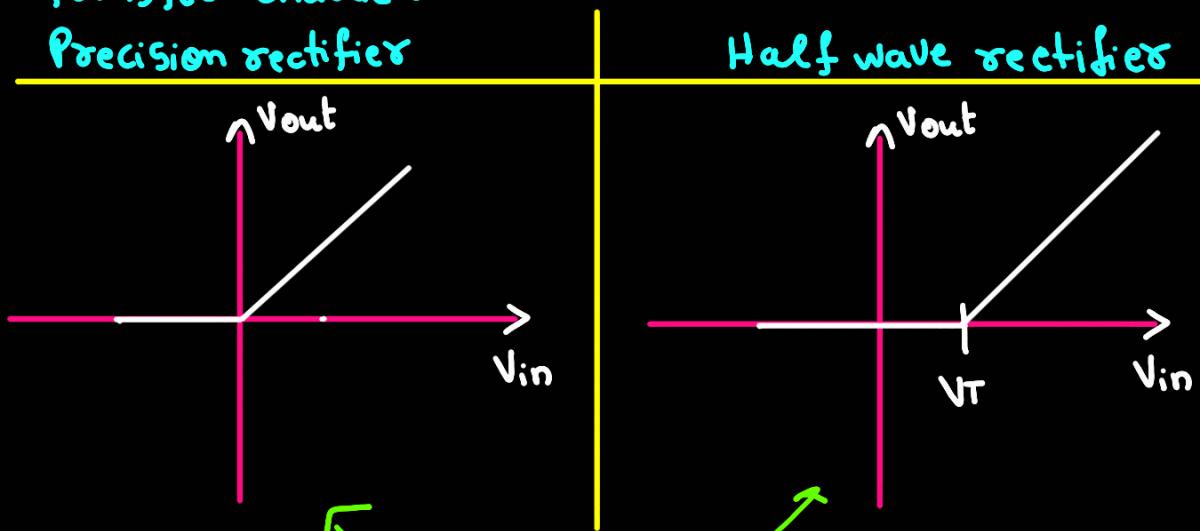

That's why Precision Rectifier
is called super diode


Working:-

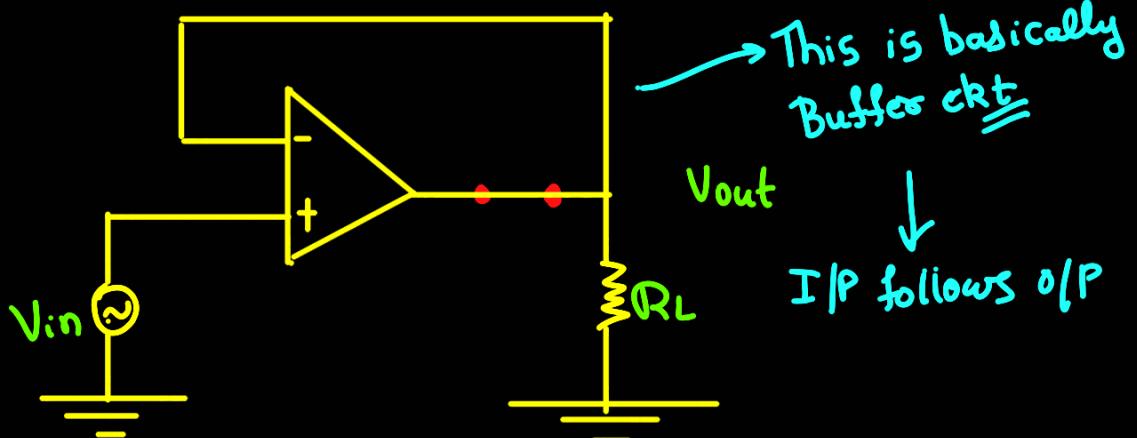When $V_{in} > 0 \Rightarrow$ diode behaves as closed switch



When $V_{in} < 0 \Rightarrow$ Simply becomes open switch

$$\hookrightarrow V_{out} = 0$$

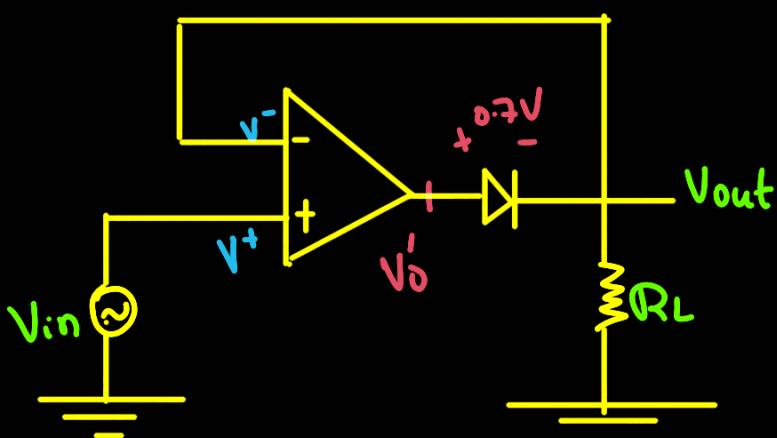

Let $V_f \Rightarrow$ Voltage drop across diode

In Closed loop configuration

$$V_d' = \frac{V_f}{A_{OL}}$$

Effective voltage drop

\uparrow Open Loop gain of the op-amp.

*Analysis for different input signals:-

Assume diode is conducting for a given i/p voltage

$$V_d' = \text{o/p voltage of op-Amp}; \overbrace{V_f = 0.7V}^{\text{Assumed Si diode is used}}$$

$$\Rightarrow V_d' = V_o + 0.7V$$

\hookrightarrow operated with -ve feedback

\hookrightarrow Virtual ground exists

$$V_d' = A_{OL} (V^+ - V^-) \Rightarrow \underbrace{V_o + 0.7V}_{A_{OL}} \approx 0 = V^+ - V^-$$

$$\Rightarrow V^+ = V^- \Rightarrow V_{out} = V_{in}$$

∴ Whenever diode is conducting $\Rightarrow V_{out}$ follows V_{in}

When $V_{in} > 0V \Rightarrow$ Diode conducts $\Rightarrow V_{out} = V_{in}$

When $V_{in} < 0V \Rightarrow$ Diode does not conduct \Rightarrow Op-Amp goes into -ve saturation with some $-V_{sat}$


When V_{in} becomes $> 0V \Rightarrow$ Op-Amp needs
to come out of
negative saturation voltage

Not a problem when operated at low frequencies. (50-100Hz)

↓
Operated at high freq \Rightarrow Op-Amp becomes distorted

↳ Prevention is done as follows:-


Modified Precision Rectifier :-

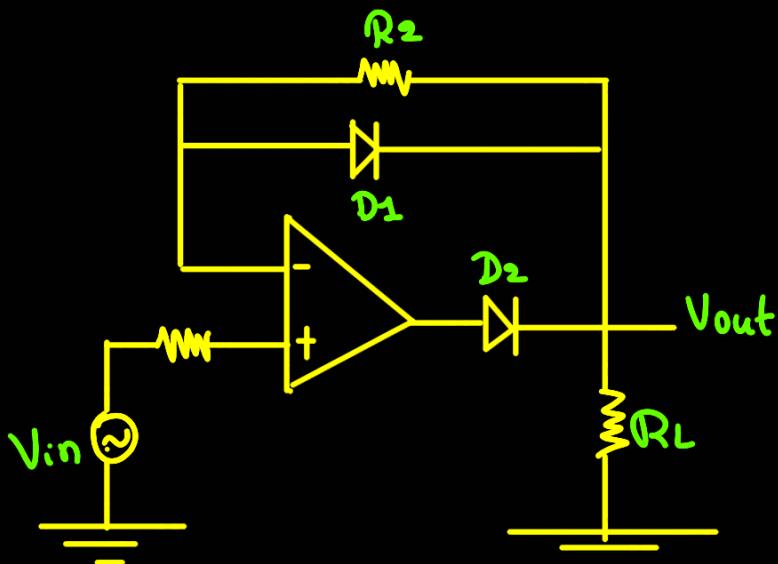


$$V_{in} > 0 \Rightarrow V_o = 0$$

$$V_{in} < 0 \Rightarrow V_o = -\frac{R_2}{R_1 + R_2} \times V_{in} \Rightarrow \text{Thus prevents } V_o \text{ from going into -ve saturation}$$


Wein Bridge Oscillator:-

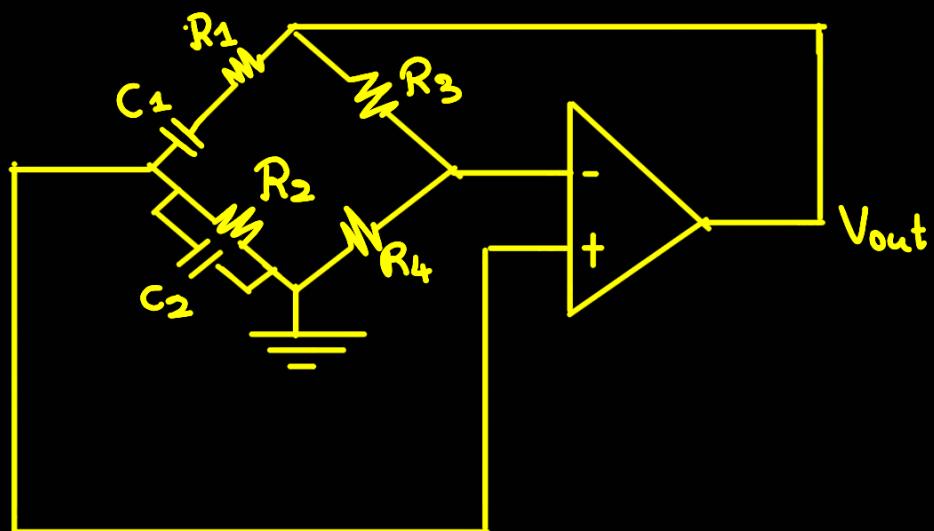

Redrawing this, we get

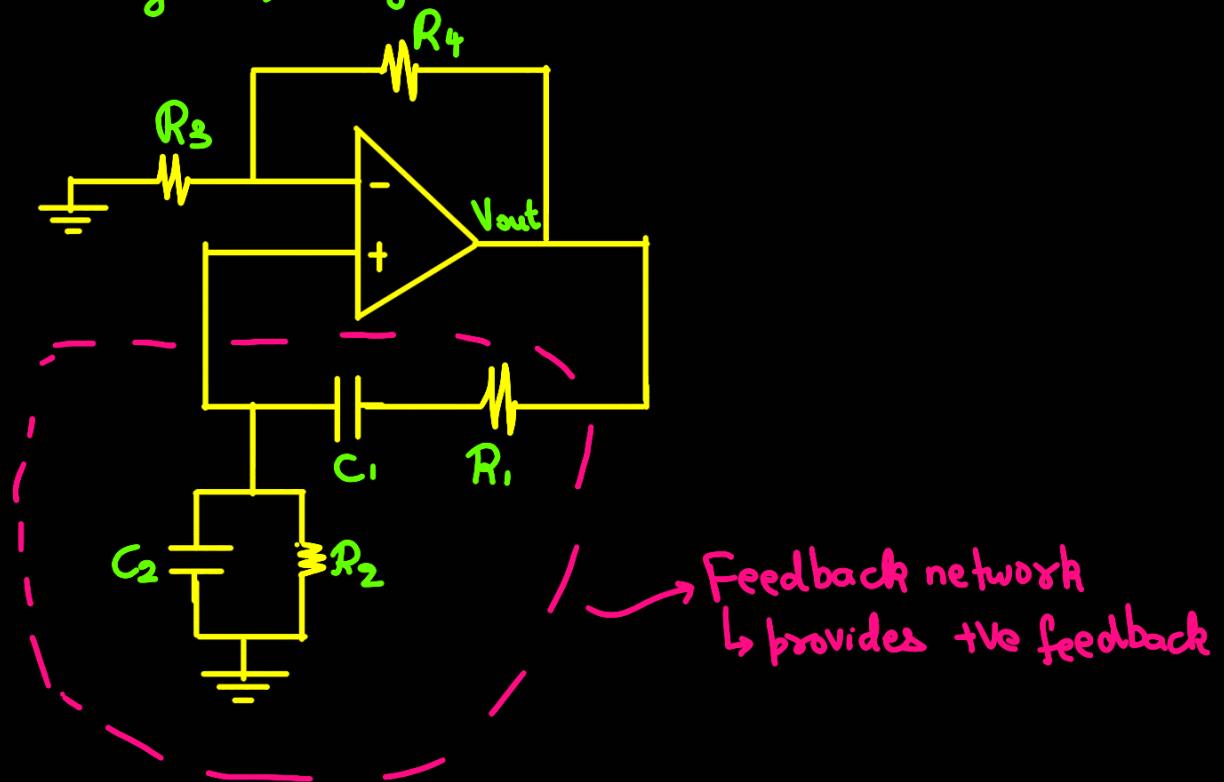

Consider the feedback network:-

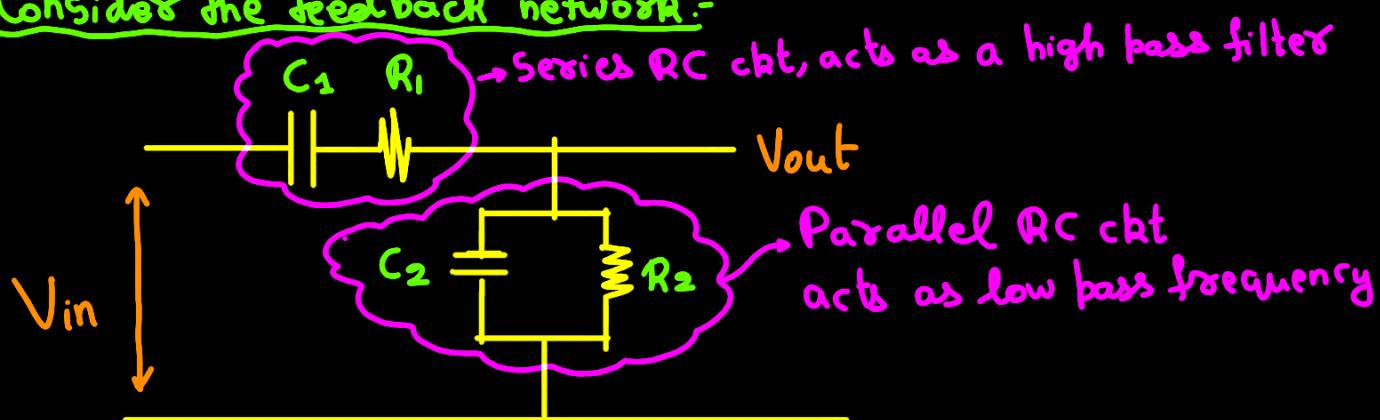

$f_r \rightarrow$ resonant frequency

Response at $f_r \rightarrow$ 

At f_r , phase shift $\phi = 0$ & $\frac{V_o}{V_{in}} = \frac{1}{3}$

If $R_1 = R_2 \& C_1 = C_2$, then:-

$$f_r = \frac{1}{2\pi RC}$$

RC Phase Shift oscillator


Either works ^{check gain}

Same as AEC, replace BJT with inverting or non-inverting amp.

Schmitt Trigger:


Not immune to noise

Consider the following ¹ Comparator:-

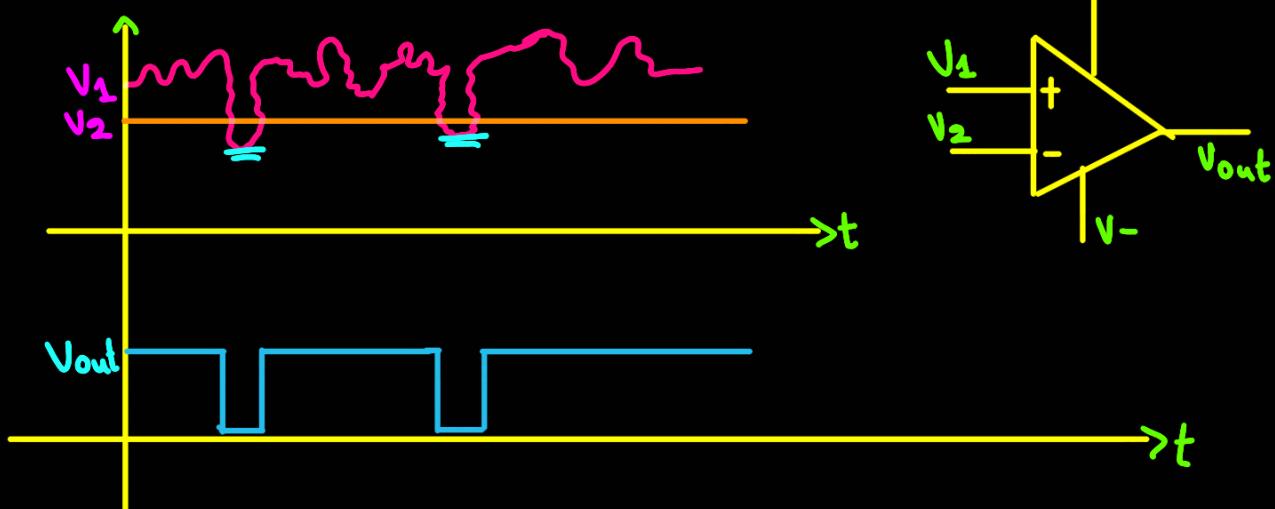

At two instances, $V_1 < V_2$ due to noise, $\therefore V_{out}$ gets affected
 ζ is low for that duration

This is fixed by Schmitt Trigger

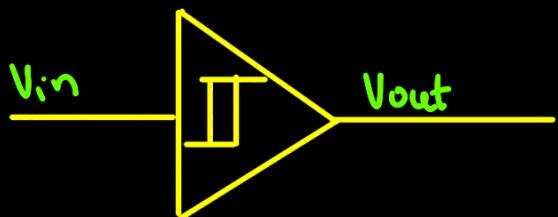


ComPARATOR with Hysteresis

→ Has 2 threshold voltages

 ↳ Upper $V_T \geq$ Low to High Transition

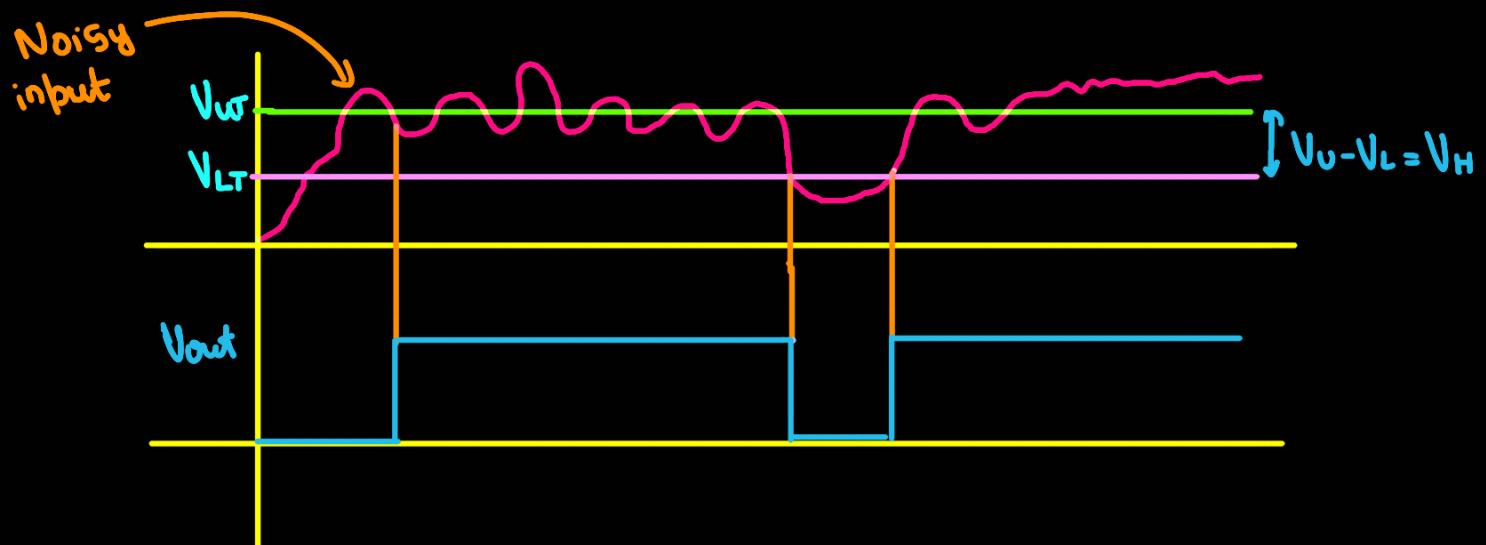 ↳ Lower $V_T \geq$ High to Low Transition



OP is low until input voltage is lower than V_{LT} . Remains high until it goes below V_{UT}


$V_U - V_L = V_H \rightarrow$ Hysteresis voltage of Schmitt Trigger
↳ Defines its noise immunity

4 parameters are needed to define Schmitt Trigger


1. High op level
2. Low op level
3. Lower threshold Voltage
4. Upper Threshold voltage

★ Transfer characteristic of Schmitt Trigger. ↗ AKA Hysteresis Curve


Non-inverting
Schmitt
Trigger

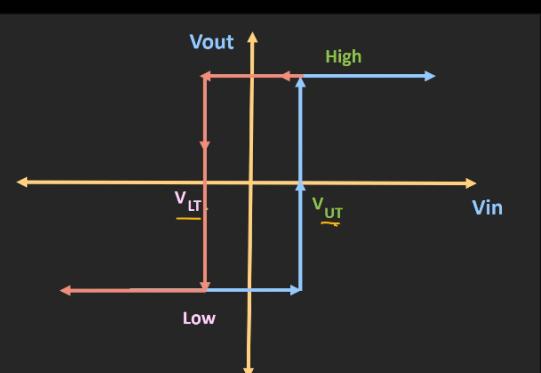

Inverting

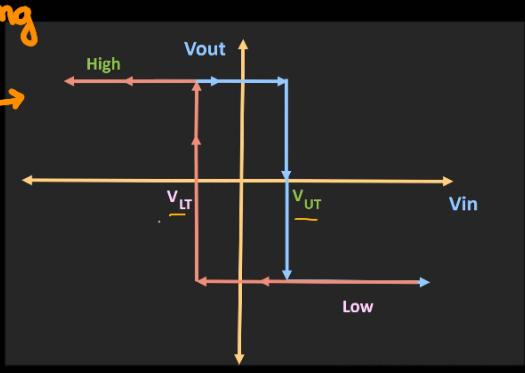

Inverting Schmitt Trigger :-

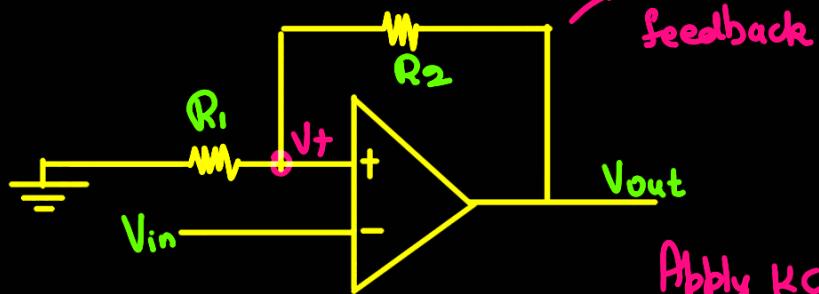

Apply KCL

$$\frac{V_+ - 0}{R_1} + \frac{V^+ - V_{out}}{R_2} = 0$$

$$V_{in} > V_+ \Rightarrow V_{out} = V_L$$

$$V_{in} < V_+ \Rightarrow V_{out} = V_H$$

$$V_+ = \frac{R_1}{R_1 + R_2} V_{out}$$

$$V_L = \frac{R_1}{R_1 + R_2} \times V_H$$

$$V_{in} > V_L \Rightarrow V_{out} = V_L$$

$$V_{UR} = \frac{R_1}{R_1 + R_2} \times V_H$$


Upper threshold voltage

When $V_{in} < V_+$

at that point $V_+ = V_2 \Rightarrow V_2 = \frac{R_1}{R_1 + R_2} \times V_L \rightarrow$ Lower threshold voltage

$$V_{LT} = \frac{R_1}{R_1 + R_2} \times V_L$$

Non-inverting Schmitt Trigger :-

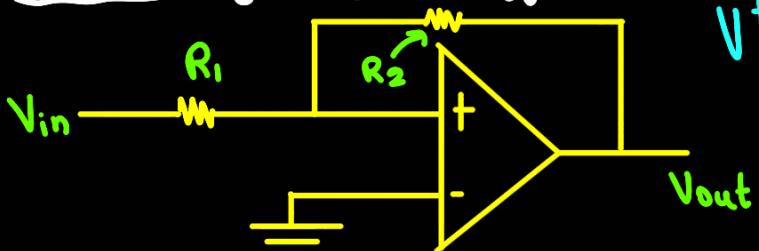

Derive from KCL

$$V^+ = \frac{R_2}{R_1 + R_2} V_{in} + \frac{R_1}{R_1 + R_2} V_{out}$$

$$V_{in} > 0 \Rightarrow V_{out} = V_H$$

Condⁿ :-

Upper threshold voltage

$$V_{in} > -\frac{R_1}{R_2} V_L \Rightarrow V_{UR} = -\frac{R_1}{R_2} \times V_L$$

$$V_{in} < 0 \Rightarrow V_{out} = V_L$$


Condⁿ :-

Lower threshold voltage


$$V_{in} < -\frac{R_1}{R_2} V_H \Rightarrow V_{LT} = -\frac{R_1}{R_2} \times V_H$$

Astable Multivibrator :-

Used to design relaxation oscillator

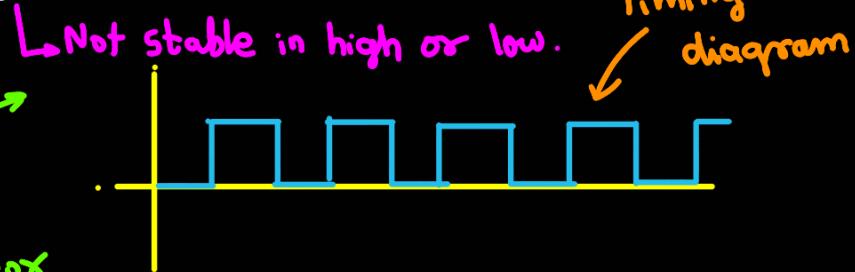

Design using Op-Amp

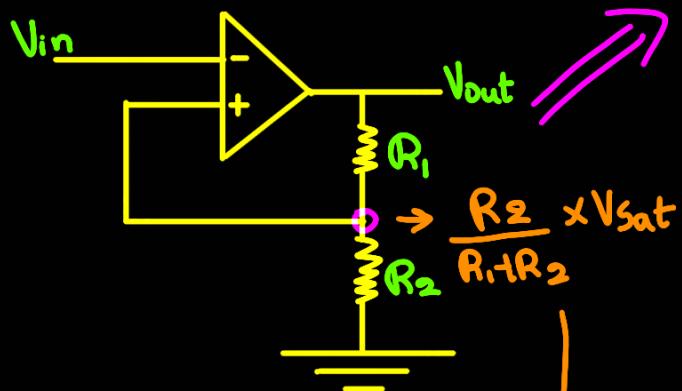

Schmitt trigger dkt.

↳ Basic astable vibrator dkt is similar

Let, initially, $V_{out} = +V_{sat}$

βV_{sat}
feedback fraction

If $V_{in} < \beta V_{sat} \Rightarrow V_{out} = +V_{sat}$

When $V_{in} > \beta V_{sat} \Rightarrow V_{out} = -V_{sat}$

@ that time, $V^+ = -V_{sat} \times \frac{R_2}{R_1+R_2} = -\beta V_{sat}$

Transfer characteristics:- Same as inverting Schmitt Triggered

Some explanation


$$V_{LT} = -\beta V_{sat} \quad V_{UT} = \beta V_{sat}$$

$$\text{Hysteresis} = V_{UT} - V_{LT}$$


Schmitt Trigger \Rightarrow External input

Astable Vibrator \Rightarrow Feedback is fed back to i/p using R & C

The ONLY difference in dkt

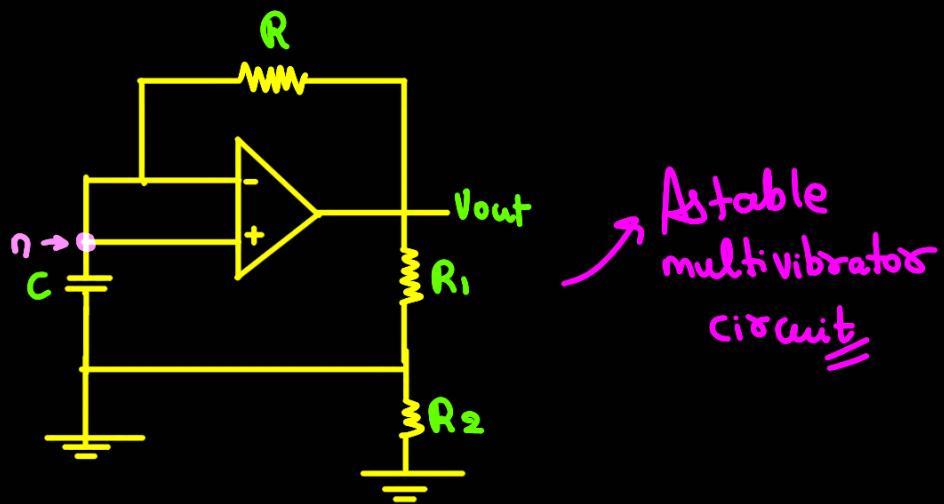

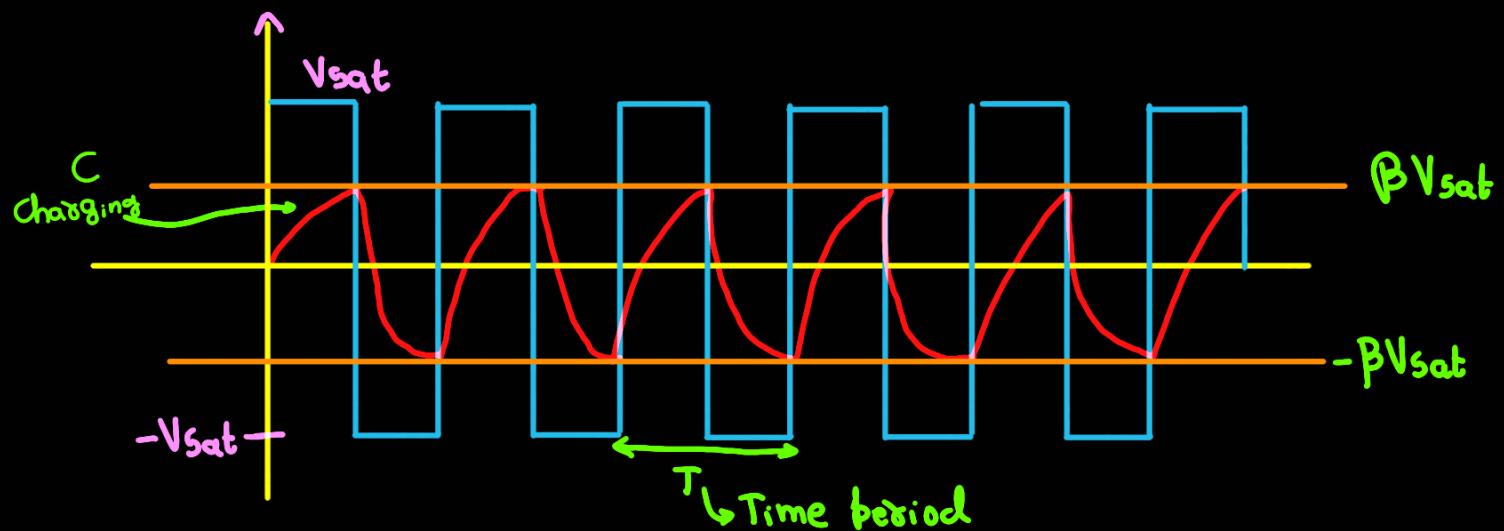Working principle:- Initially $V_0 = +V_{sat}$ (assumed)



* At the start, capacitor starts charging to V_{sat} . Voltage gets built up across the capacitor.

* Voltage at node n also gets built up.

* Once Capacitor charges to $V_{LT} = \beta V_{sat}$, Op-Amp o/p switches from $+V_{sat}$ to $-V_{sat}$

* The capacitor charges to $-V_{sat} = V_{LT}$. Upon reaching, o/p switches to $+V_{sat}$


* Time period $T \Rightarrow$ depends on $R, C, V_{LT} \leq V_{LT} \geq R_1 \leq R_2$

$$T = 2RC \log_e \left(\frac{1+\beta}{1-\beta} \right)$$

If $V_{sat} = -V_{sat}$
Duty Cycle = 50%

Derivation for T :-

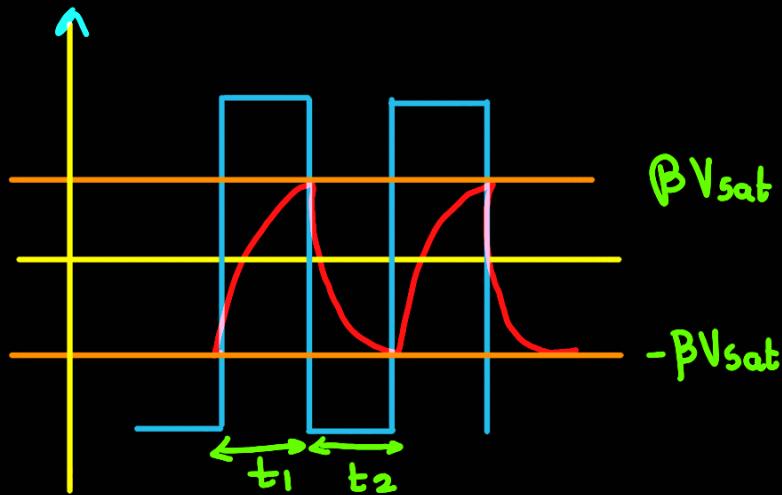Consider steady state condⁿ for the given ckt.



From transient analysis:-

$$V_c(t) = V_{\text{Final}} + [V_{\text{Initial}} - V_{\text{Final}}] e^{-t/RC}$$

$$\left. \begin{array}{l} V_{\text{final}} = V_{\text{sat}} \\ V_{\text{in}} = -\beta V_{\text{sat}} \end{array} \right\} V_c(t_1) = V_{\text{sat}} + [-\beta V_{\text{sat}} - V_{\text{sat}}] e^{-t_1/RC}$$

$$\beta V_{\text{sat}} = V_{\text{sat}} - [1 + \beta] V_{\text{sat}} e^{-t_1/RC}$$

$$\beta - 1 = -[1 + \beta] e^{-t_1/RC} \Rightarrow \left(\frac{1 - \beta}{1 + \beta} \right) = -e^{t_1/RC}$$

$$t_1 = RC \ln \left(\frac{1 + \beta}{1 - \beta} \right)$$

\therefore Duty Cycle = 50%

$$\text{Intuitively } t_2 = RC \ln \left(\frac{1 + \beta}{1 - \beta} \right)$$



$$\therefore T = t_1 + t_2 = 2RC \ln \left(\frac{1 + \beta}{1 - \beta} \right)$$

Ques:- Design an astable multivibrator for $f = 1 \text{ kHz}$. Assume $R_1 = R_2 = R$ & $C = 0.1 \mu\text{F}$


Monostable Vibrator :-

- One state is stable state
- When trigger signal is applied \Rightarrow O/P goes to unstable state momentarily

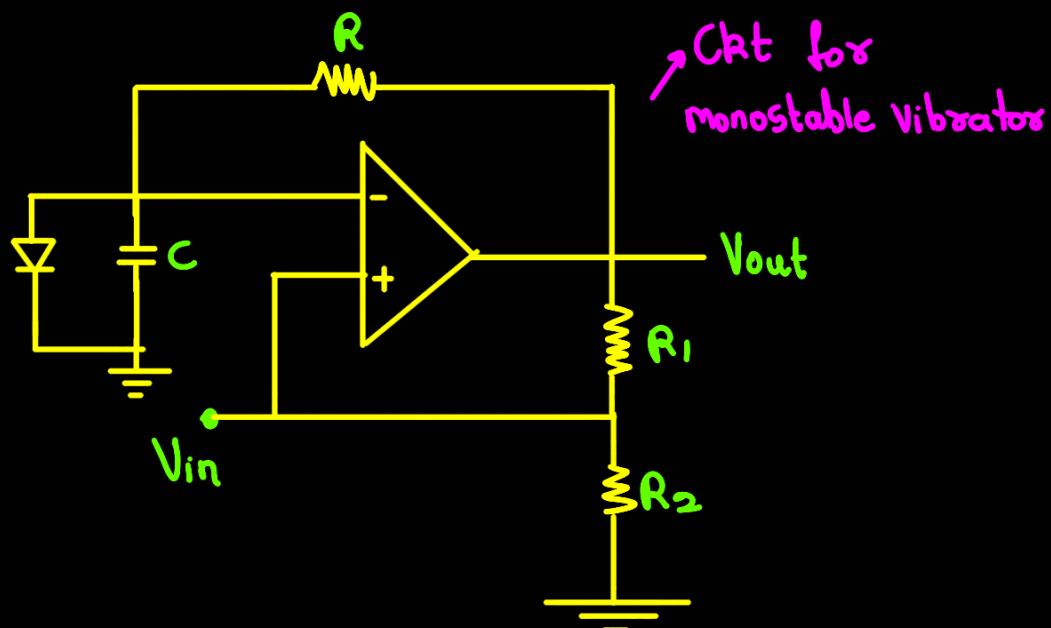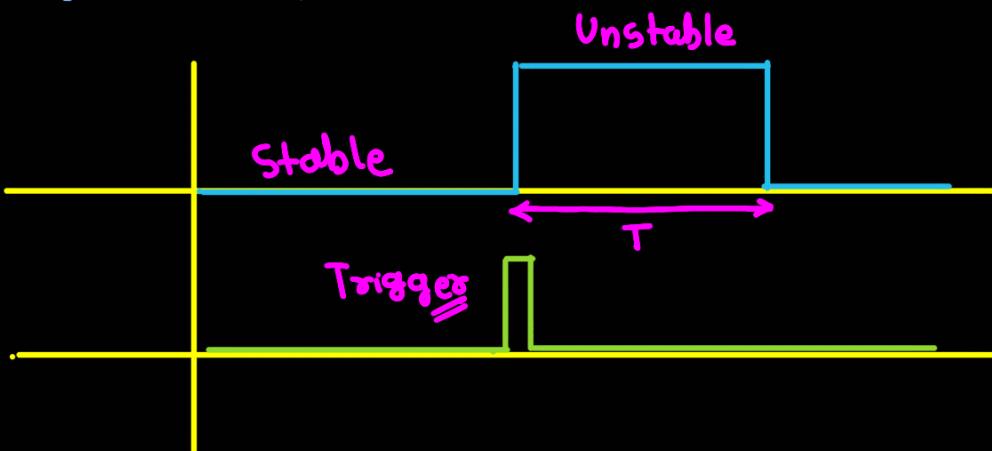- After time T , it reverts back to stable state




Working Principle :-

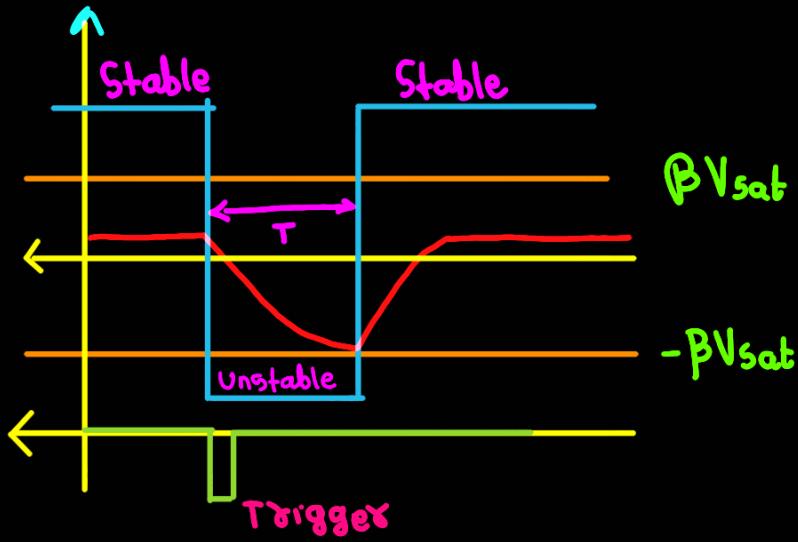

$$T = RC \ln\left(1 + \frac{R_2}{R_1}\right)$$

Derivation for T:-

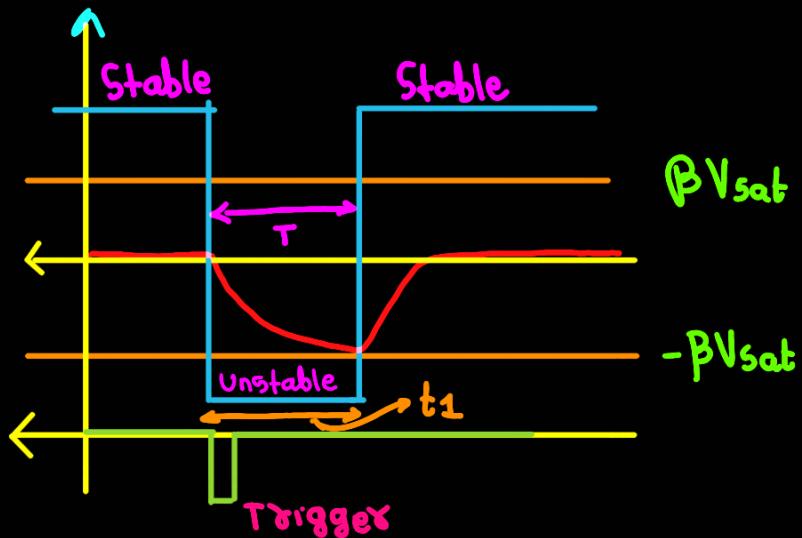

BV_{sat}

$-BV_{sat}$

Assumption:- diode is ideal \Rightarrow drop across capacitor is ≈ 0

From transient analysis:-

$$V_c(t) = V_{final} + (V_{initial} - V_{final}) e^{-t/RC}$$

$$V_{final} = -V_{sat} ; V_{initial} = 0V$$

$$V_c(t_1) = -V_{sat} + (0 - (-V_{sat})) e^{-t_1/RC}$$

$$-BV_{sat} = -V_{sat} + V_{sat} e^{-t_1/RC}$$

$$\therefore 1 - \beta = e^{-t_1/RC} \quad \left(\because WKT, \beta = \frac{R_2}{R_1 + R_2} \right)$$

$$1 - \frac{R_2}{R_1 + R_2} = e^{-t_1/RC} \Rightarrow \frac{R_1}{R_1 + R_2} = e^{-t_1/RC}$$

Time period of triggers must be very small comp. to T of unstable mode

$$\therefore t_1 = -RC \ln\left(\frac{R_1}{R_1 + R_2}\right) \Rightarrow t_1 = RC \ln\left(1 + \frac{R_2}{R_1}\right)$$

How to generate triggers? \rightarrow Using RC differentiator circuit



∴ Overall structure for monostable vibrator:-

